

# Lecture 02: Ratioless Logic Designs

Prof. Ming-Bo Lin

Department of Electronic Engineering

National Taiwan University of Science and Technology





## Syllabus

- Basic operations of switches
- Switch logic circuits
- Systematic design methodologies

# Syllabus


- Basic operations of switches
  - nMOS switches
  - pMOS switches
  - TG switches
  - Basic logic circuits
- Switch logic circuits
- Systematic design methodologies

# nMOS Switches

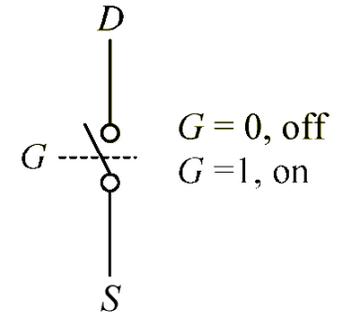
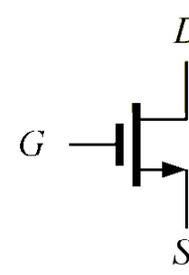
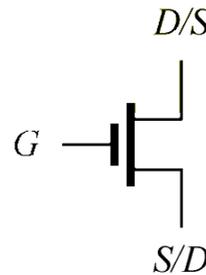
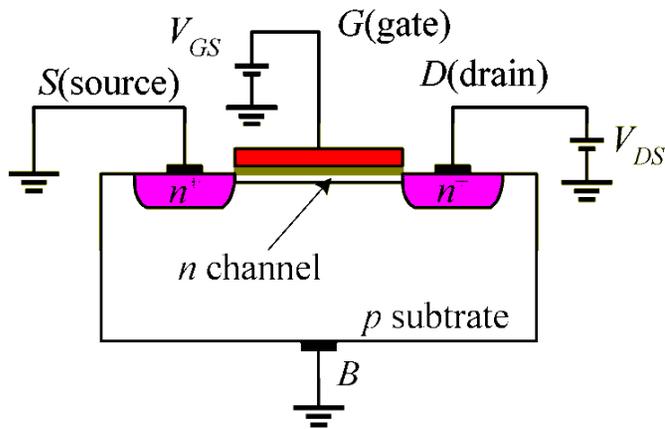


$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ \left( V_{GS} - V_{T,n} - \frac{1}{2} V_{DS} \right) V_{DS} \right]$$
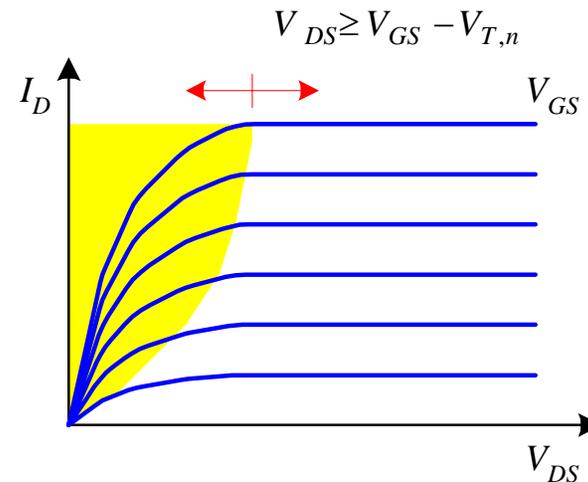
$$I_{D,sat} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{T,n})^2$$






# nMOS Switches

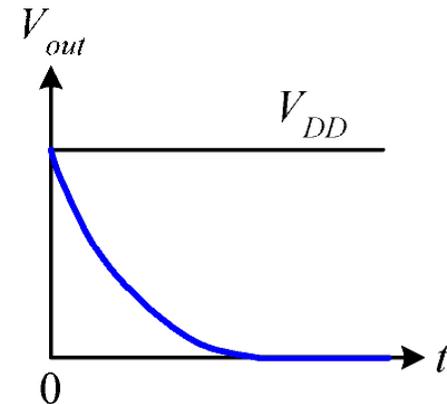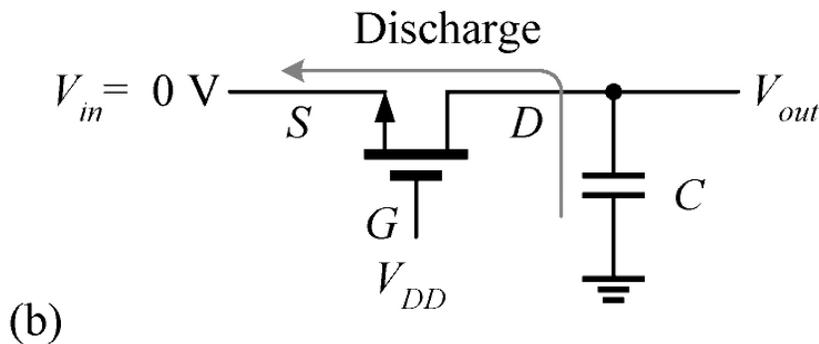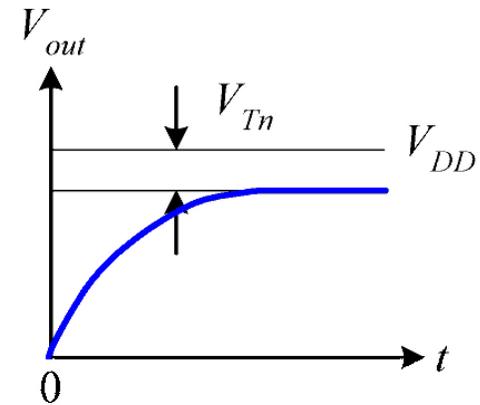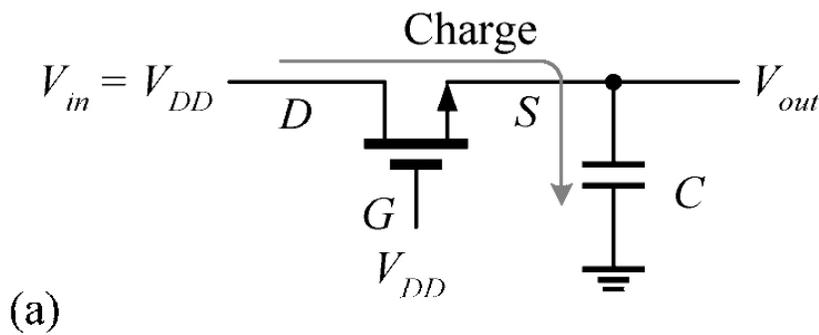

# Syllabus


- Basic operations of switches
  - nMOS switches
  - pMOS switches
  - TG switches
  - Basic logic circuits
- Switch logic circuits
- Systematic design methodologies

# pMOS Switches


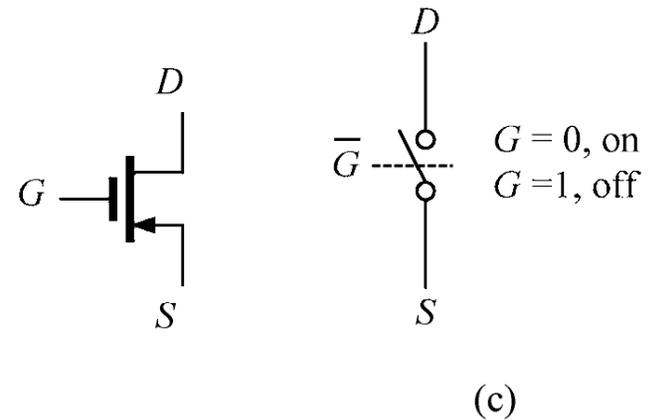
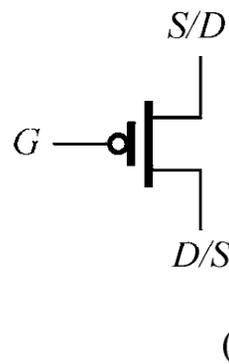
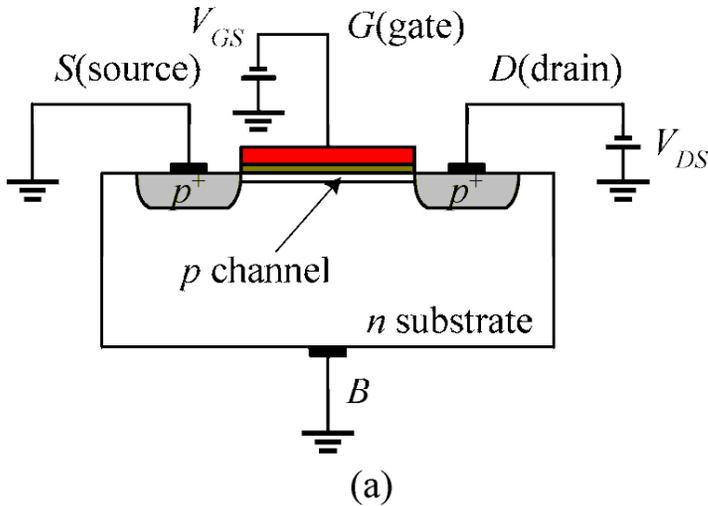


$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ \left( V_{SG} - |V_{T,p}| - \frac{1}{2} V_{SD} \right) V_{SD} \right]$$

$$I_{D,sat} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( V_{SG} - |V_{T,p}| \right)^2$$

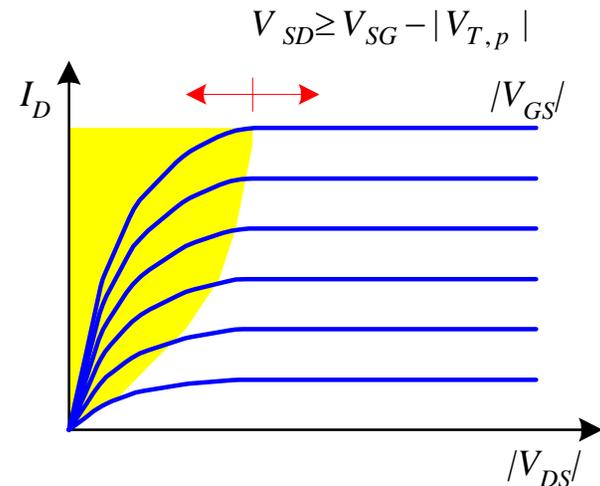



# pMOS Switches

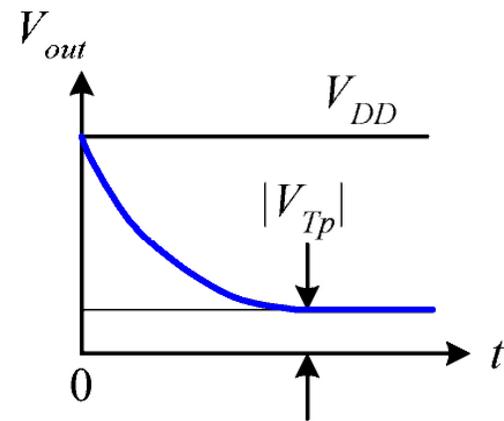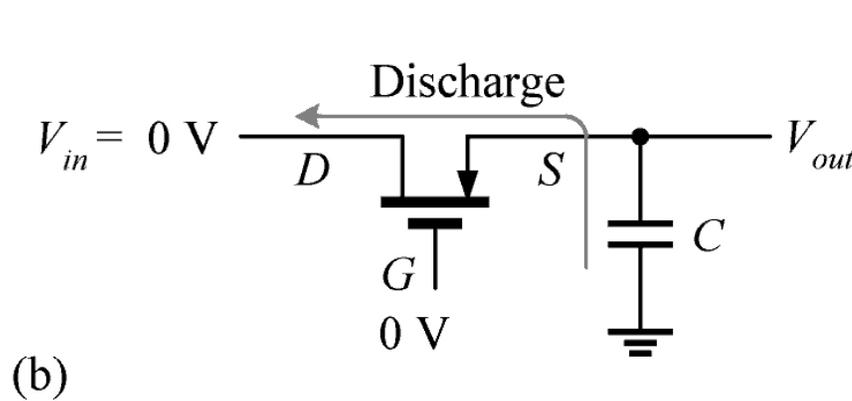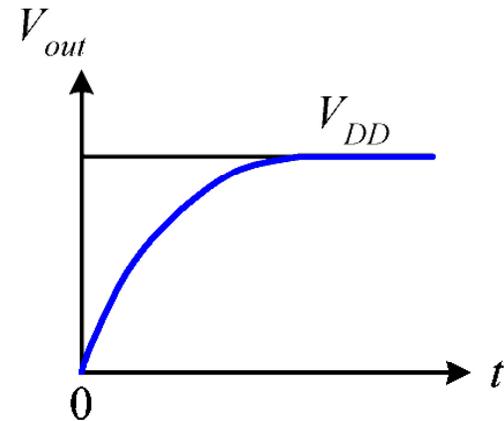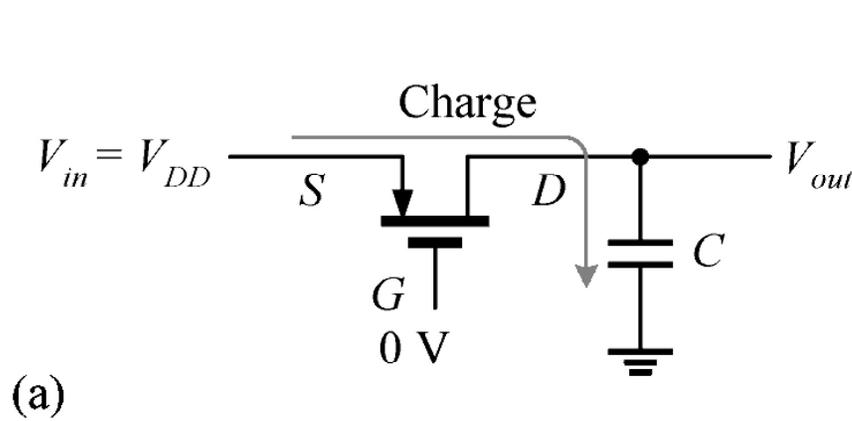



# Syllabus

- Basic operations of switches
  - nMOS switches
  - pMOS switches
  - TG switches
  - Basic logic circuits
- Switch logic circuits
- Systematic design methodologies

# TG Switches

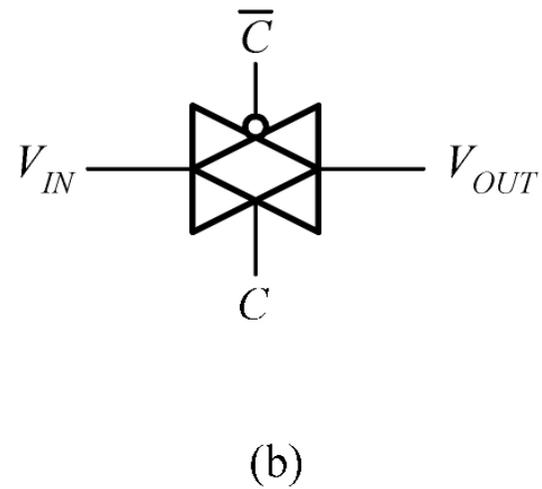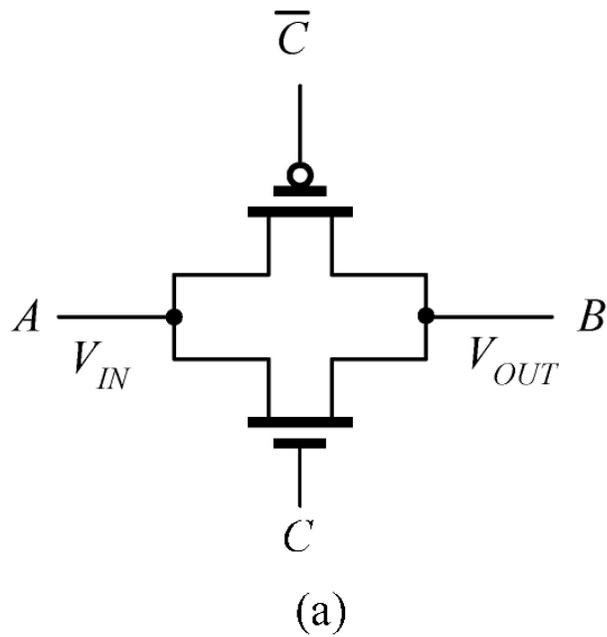


# TG Switches

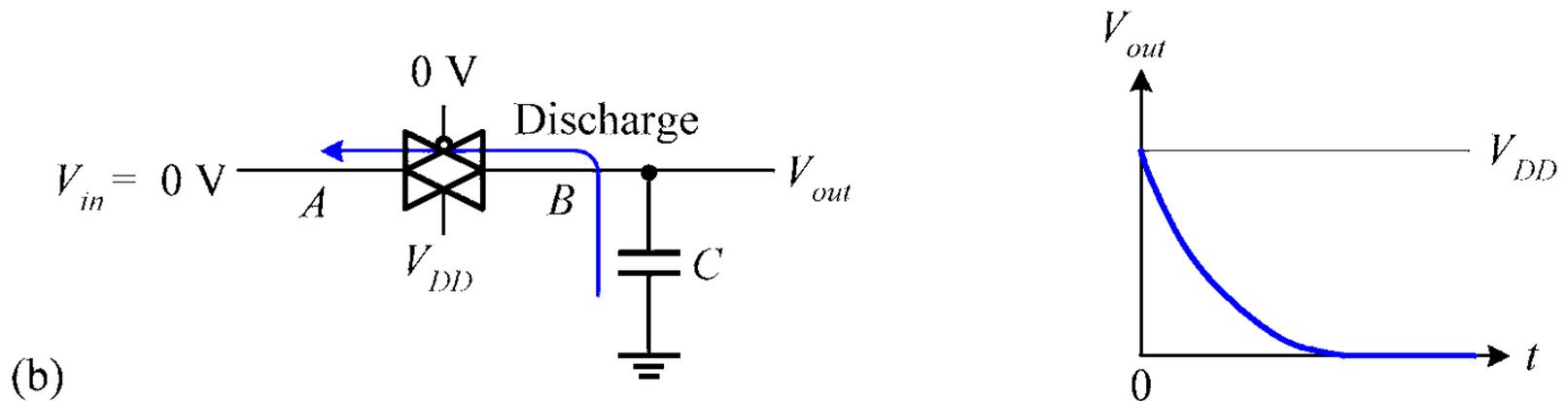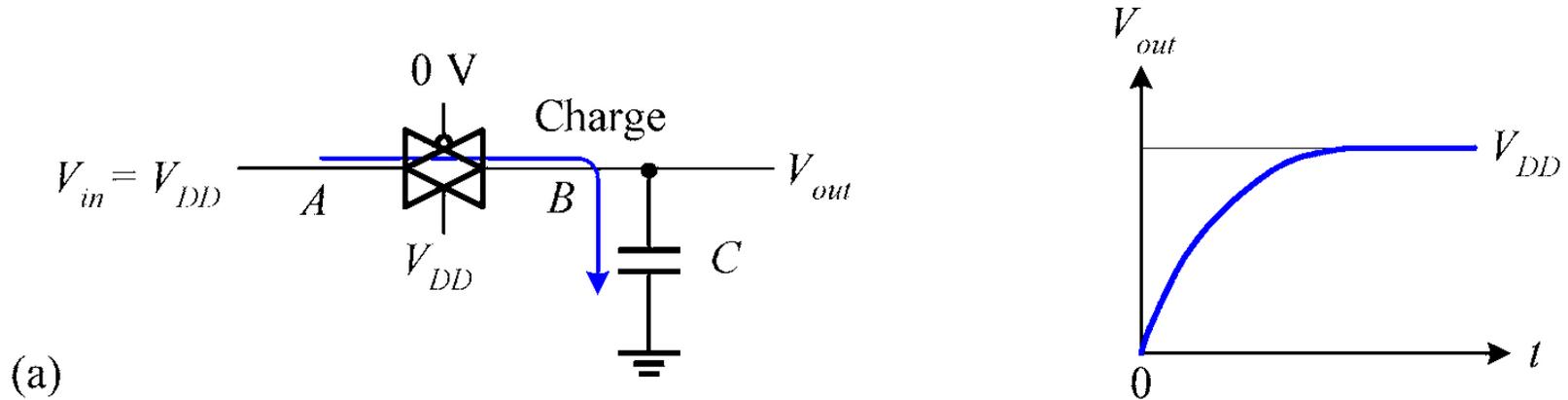


# Syllabus

- Basic operations of switches
  - nMOS switches
  - pMOS switches
  - TG switches
  - Basic logic circuits
- Switch logic circuits
- Systematic design methodologies

# Basic Logic Circuits

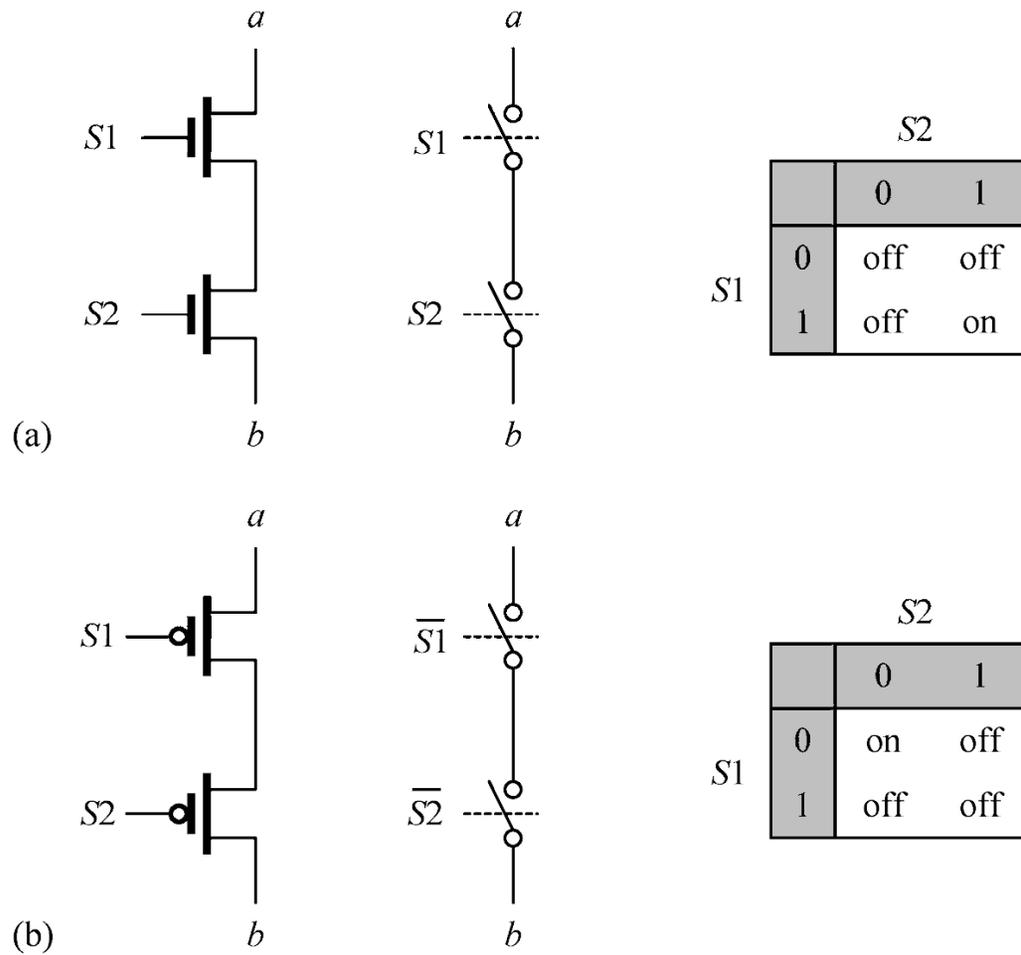


# Basic Logic Circuits

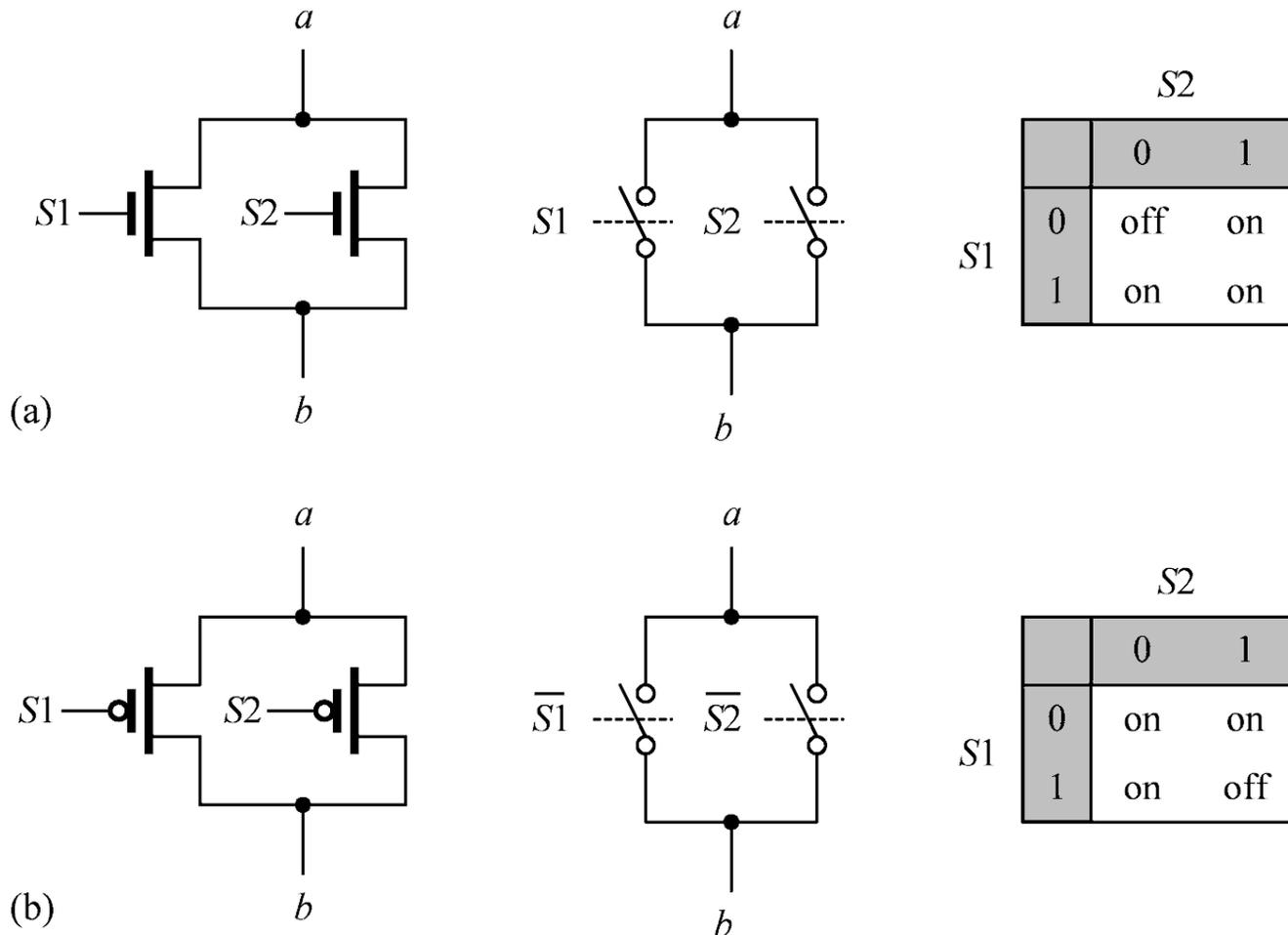

## $f/f'$ Implementation

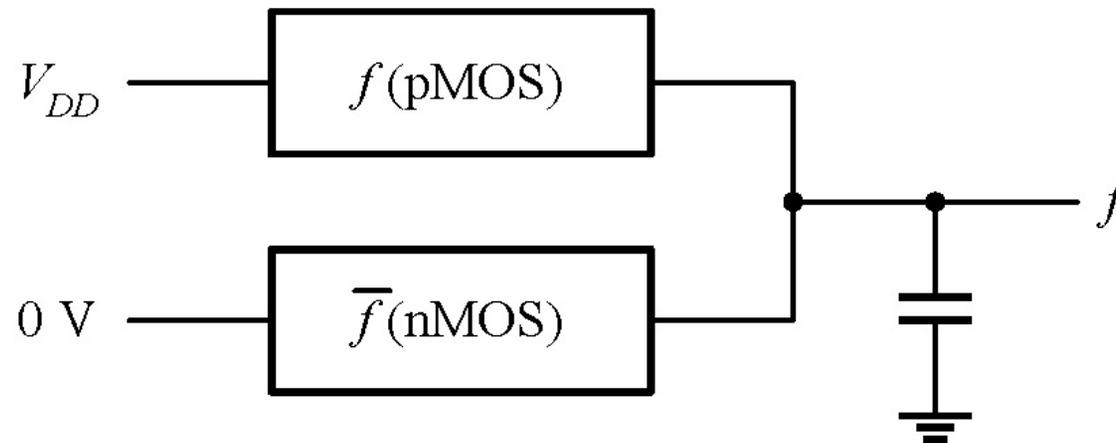
### ■ $f/f'$ implementation (FCMOS)

- $f$  function (pull-up network (PUN))
- $f'$  function (pull-down network (PDN))




# $f/f'$ Implementation

- A two-input NAND gate example

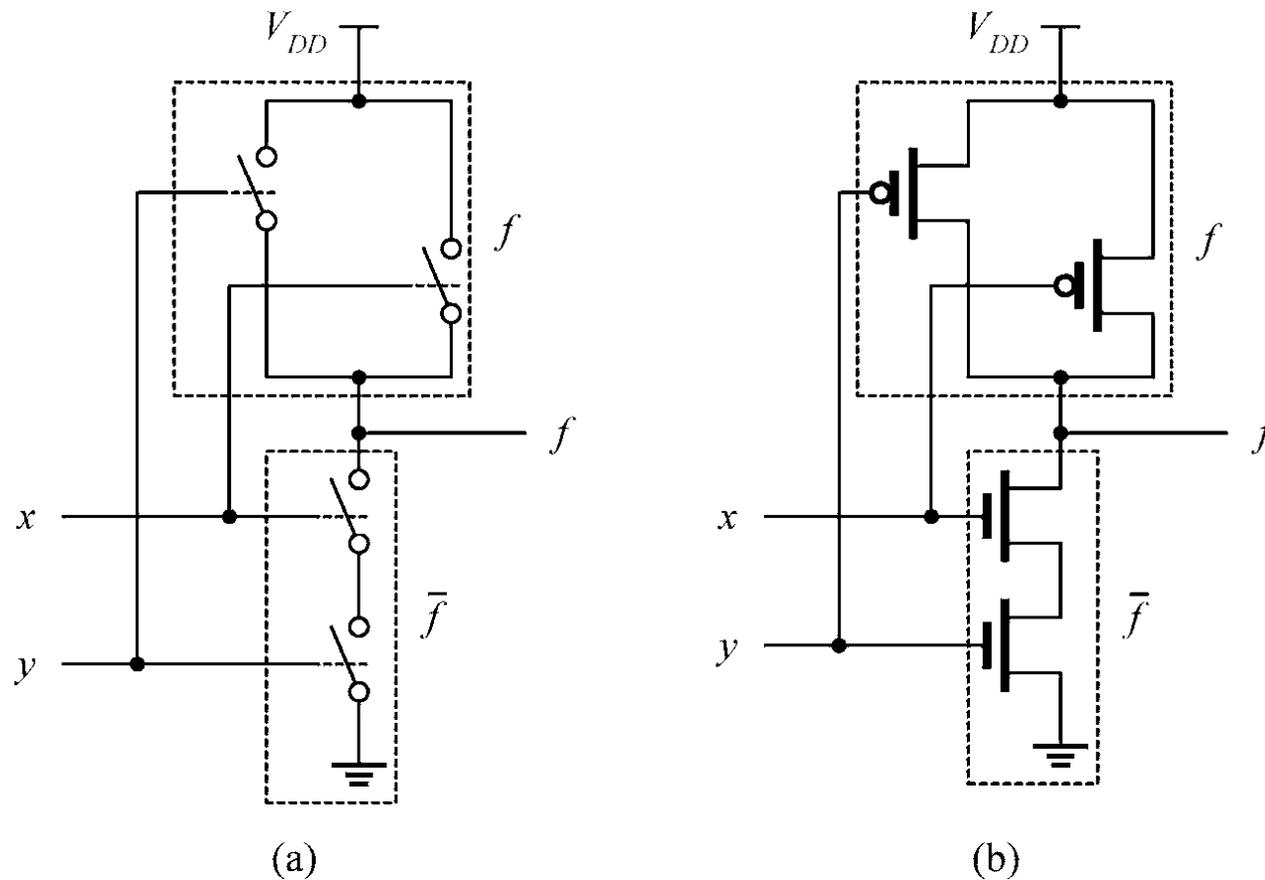

# $f/f$ Implementation

## ■ AND-OR-Inverter (AOI)

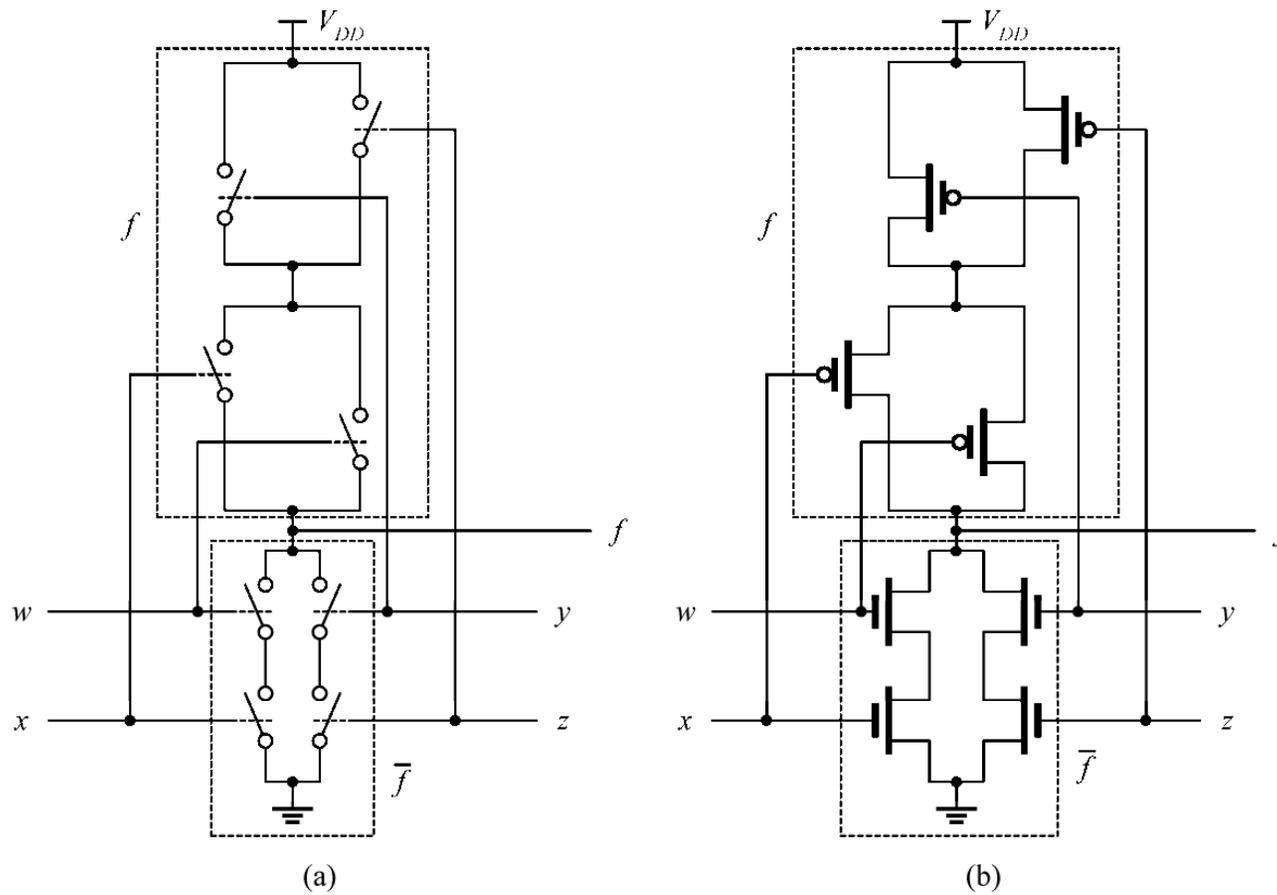


# Syllabus


- Basic operations of switches
- Switch logic circuits
  - Switch logic circuits
  - Basic rules
  - Shannon's expansion theorem
  - Residues of a switching function
- Systematic design methodologies
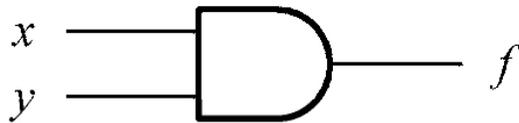
# Switch Logic Circuits

- Why the following logic circuit cannot work correctly?



(a)

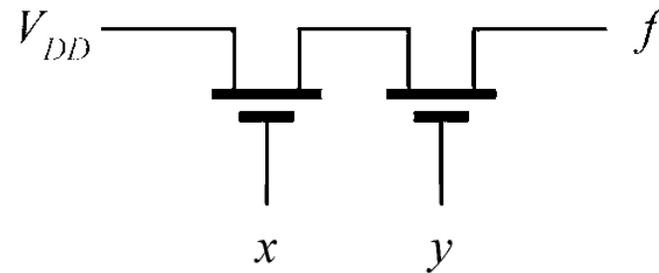


(b)

- Another example

Can the right logic circuit correctly implement the switching function?

$$f(x, y, z) = xy + yz + yz$$

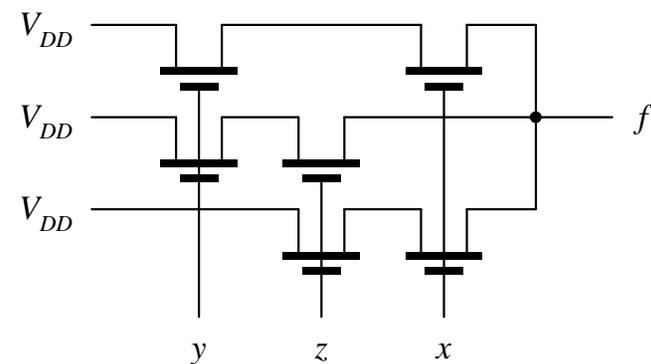

# Syllabus

- Basic operations of switches
- Switch logic circuits
  - Switch logic circuits
  - Basic rules
  - Shannon's expansion theorem
  - Residues of a switching function
- Systematic design methodologies

## Basic Rules

### ■ Rule 1 (node-value rule)

- The function or a signal summing point must **always** be connected to 0 **or** 1 at any time

### ■ Rule 2 (node-conflict-free rule)

- The function or a signal summing point must **never** be connected to 0 **and** 1 at the same time

Please always remember these two rules.

## Basic Rules

### ■ Rule 1

- Correct logic function

### ■ Rule 2

- Distinguishes ratioless logic from ratioed logic

### ■ Ratioless logic

- Both rules are confined

### ■ What is ratioless logic?

## Syllabus


- Basic operations of switches
- Switch logic circuits
  - Switch logic circuits
  - Basic rules
  - Shannon's expansion theorem
  - Residues of a switching function
- Systematic design methodologies

# Shannon's Expansion Theorem

## ■ Shannon's expansion theorem

$$f(x_{n-1}, x_{n-2}, \dots, x_2, x_1, x_0) = x_i f(x_{n-1}, x_{n-2}, \dots, x_{i+1}, 1, x_{i-1}, \dots, x_2, x_1, x_0) + \bar{x}_i f(x_{n-1}, x_{n-2}, \dots, x_{i+1}, 0, x_{i-1}, \dots, x_2, x_1, x_0)$$

Proof: **Trivial.**

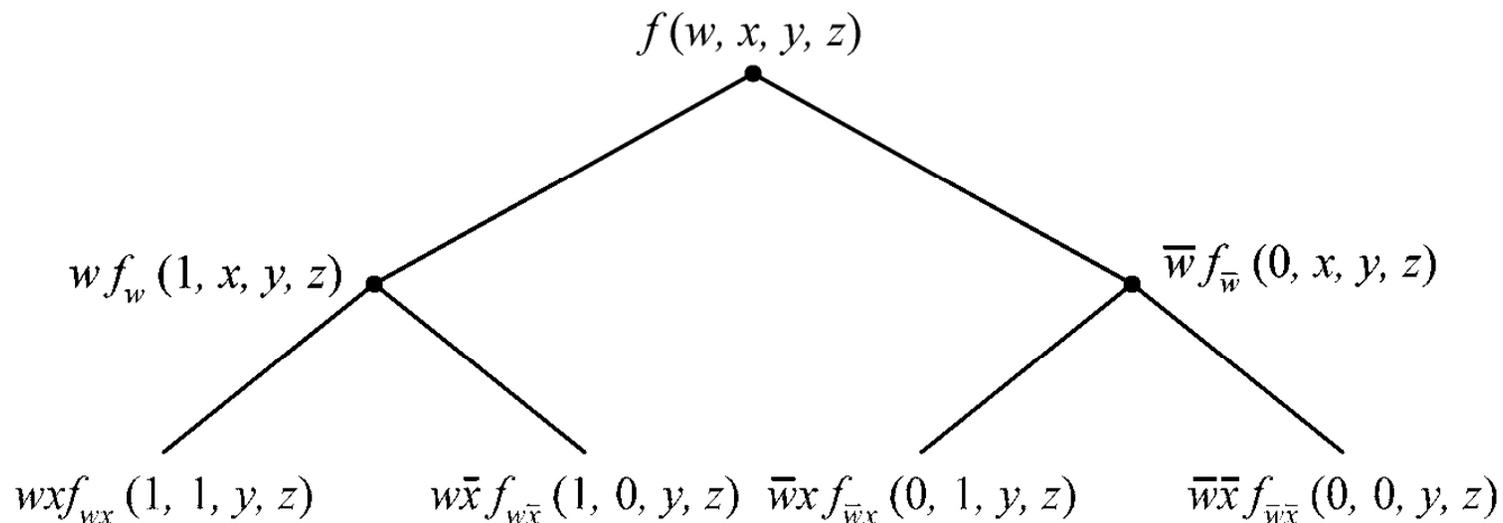

## Shannon's Expansion Theorem

### ■ An example

$$\begin{aligned}f(x, y, z) &= xy + xz + yz \\ &= \bar{x} \cdot f(0, y, z) + x \cdot f(1, y, z) \\ &= \bar{x} \cdot (yz) + x \cdot (y + z + yz) \\ &= \bar{x}yz + xy + xz\end{aligned}$$

# Syllabus

- Basic operations of switches
- Switch logic circuits
  - Switch logic circuits
  - Basic rules
  - Shannon's expansion theorem
  - Residues of a switching function
- Systematic design methodologies

## Residues of a Switching Function

■ Let

$$X = \{x_{n-1}, x_{n-2}, \mathbf{K}, x_2, x_1, x_0\}$$

$$Y = \{y_{m-1}, y_{n-2}, \mathbf{K}, y_2, y_1, y_0\}$$

For all  $y_j \in X$

■ **Residue** of  $f(X)$  with respect to  $Y$ , denote  $f_Y(X)$

- Set all **complementary** literals equal to 0
- Set all **true** literals equal to 1

## Residues of a Switching Expression

### ■ Example

$$f(w, x, y, z) = \bar{w}\bar{x}y + \bar{w}xy + \bar{w}x\bar{y}z + wxyz + (w\bar{x}y)$$

$$f_{\bar{w}\bar{x}\bar{y}}(0, 0, 0, z) = 0 \quad f_{w\bar{x}\bar{y}}(1, 0, 0, z) = 0$$


$$f_{\bar{w}\bar{x}y}(0, 0, 1, z) = 1 \quad f_{w\bar{x}y}(1, 0, 1, z) = \phi$$

$$f_{\bar{w}x\bar{y}}(0, 1, 0, z) = z \quad f_{wx\bar{y}}(1, 1, 0, z) = 0$$

$$f_{\bar{w}xy}(0, 1, 1, z) = 1 \quad f_{wxy}(1, 1, 1, z) = z$$
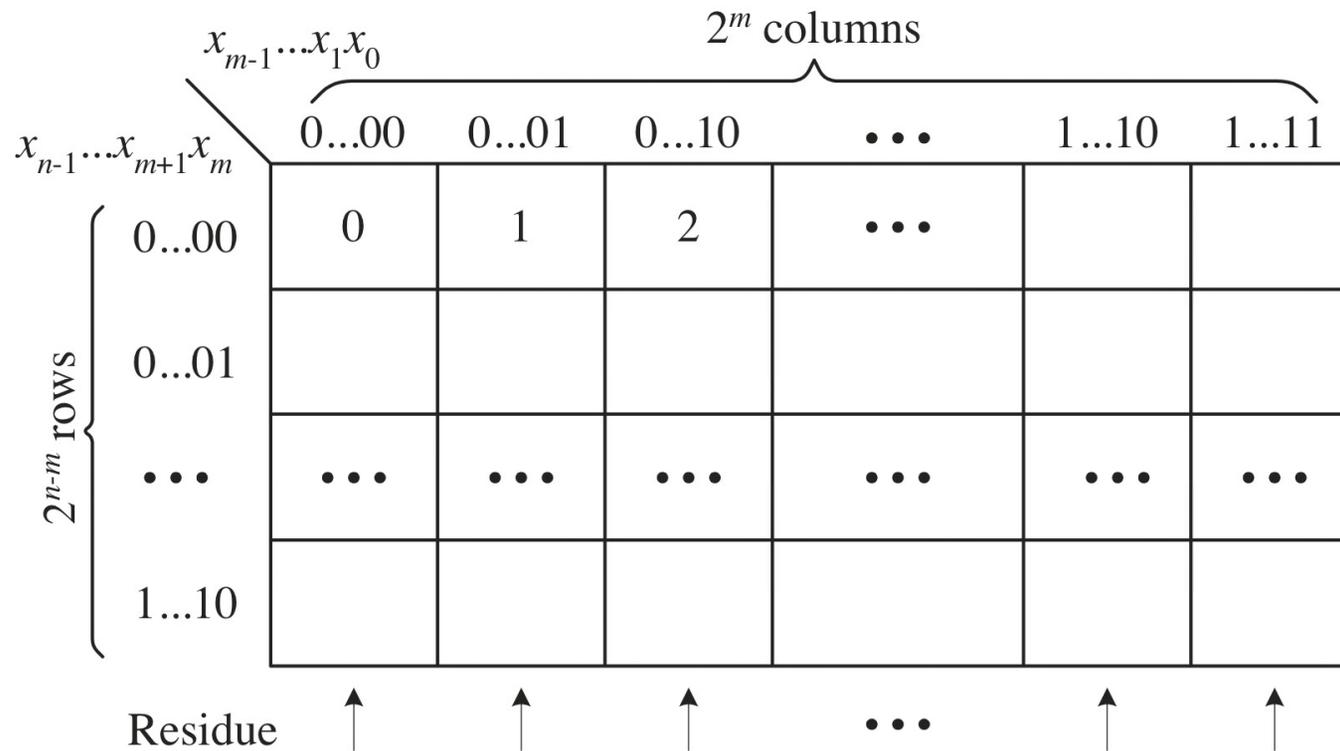
# Residue Map --- General Form

- Let  $X = \{x_{n-1}, \dots, x_1, x_0\}$   
 $Y = \{y_{m-1}, \dots, y_1, y_0\}$



## Residue Map Example

- $f(w, x, y, z) = \Sigma(0, 1, 3, 5, 6, 10, 14)$ .

$w \backslash xyz$	000	001	010	011	100	101	110	111
0	①0	①1	2	①3	4	①5	①6	7
1	8	9	①10	11	12	13	①14	15

## Residue Map Example

- $f(v, w, x, y, z) = \Sigma (1, 7, 9, 11, 13, 22, 25, 26, 27, 30, 31) + \Sigma_{\gamma} (15, 17, 19, 23)$

$vw \backslash xyz$	000	001	010	011	100	101	110	111
00	0	①	2	3	4	5	6	⑦
01	8	⑨	10	⑪	12	⑬	14	15*
11	24	⑫	⑬	⑭	28	29	⑯	⑰
10	16	17*	18	19*	20	21	⑲	23*

## Residue Map Example

■  $f(w, x, y, z) = \Sigma (0, 1, 2, 3, 4, 6, 11, 12, 15)$

$wxy$	000	001	010	011	100	101	110	111
$z$								
0	0	2	4	6	8	10	12	14
1	1	3	5	7	9	11	13	15
	↑	↑	↑	↑	↑	↑	↑	↑
	1	1	$\bar{z}$	0	0	$z$	$\bar{z}$	$z$

## Residue Map Example

$vw \backslash xyz$	000	001	010	011	100	101	110	111
00	0	①	2	3	4	5	6*	7
01	8	⑨	10	⑪	12	⑬	14*	15
11	24	⑮	⑯	⑰	28	29	30*	31
10	16	17*	18	19*	20	21	22*	23
	↑	↑	↑	↑	↑	↑	↑	↑
	0	1	$vw$	$w$	0	$\bar{v}w$	$\phi$	0

## Syllabus

- Basic operations of switches
- Switch logic circuits
- Systematic design methodologies
  - Tree network
  - 0/1- $x/x'$ -tree network
  - 0/1-tree network

## Systematic Design Methods

### ■ Tree networks

- Uniform-tree network
- Freeform-tree network

### ■ 0/1- $x/x'$ -tree network

### ■ 0/1-tree networks

- General 0/1-tree network
- $f/f'$  paradigm

## Tree Networks

### ■ Basic design method

- Repeatedly apply Shannon's expansion theorem
- Trivial literals ( $x$  and  $x'$ )


### ■ Types of tree networks

- Freeform-tree network
- Uniform- tree network


# Tree Networks
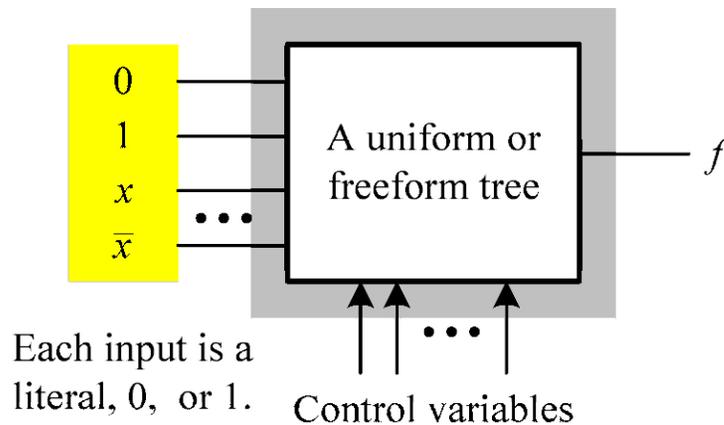
## ■ Implementations

- Using CMOS switches
- Using nMOS switches



(a) Using CMOS switches

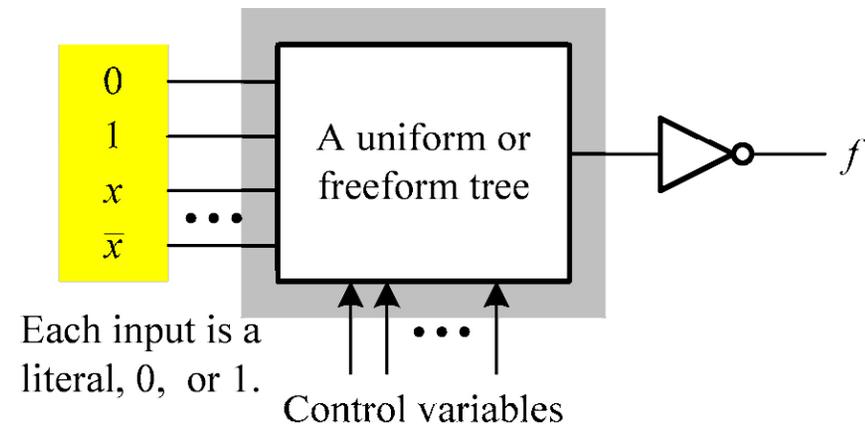

(b) Using nMOS switches

## Freeform-Tree Network


### ■ Example

$$f(w, x, y, z) = \overline{\overline{wx} + \overline{xyz} + wyz}$$

### ■ Let

$$\begin{aligned} g &= \overline{f} = \overline{\overline{wx} + \overline{xyz} + wyz} \\ &= \overline{w}(\overline{x} + x\overline{yz}) + w(\overline{xyz} + yz) \\ &= \overline{w}[\overline{x}(1) + x(\overline{yz})] + w[\overline{y}(xz) + y(z)] \\ &= \overline{w}\{\overline{x}(1) + x[\overline{y}(z) + y(0)]\} + w\{\overline{y}[\overline{x}(0) + x(z)] + y(z)\} \end{aligned}$$

# Freeform-Tree Network

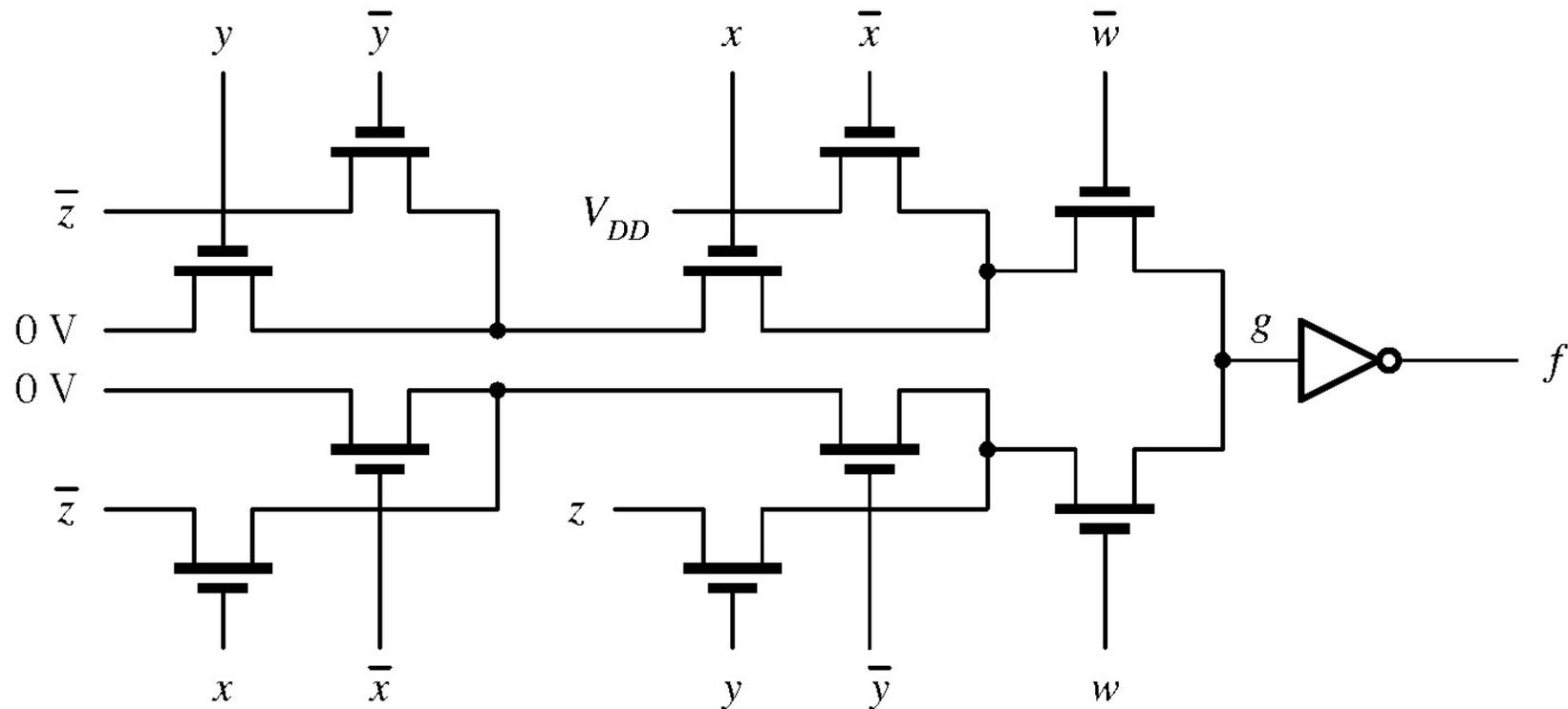

## Uniform-Tree Network


### ■ Example

$$f(w, x, y, z) = \overline{\overline{wx + xyz + wyz}}$$

### ■ Let

$$\begin{aligned} g = \overline{f} &= \overline{wx + xyz + wyz} \\ &= \overline{w(x + xyz)} + \overline{w(xyz + yz)} \\ &= \overline{w[x(1) + x(\overline{yz})]} + \overline{w[x(yz) + x(\overline{yz} + yz)]} \\ &= \overline{w\{x(1) + x[\overline{y(z)} + y(0)]\}} + \overline{w\{x\{[\overline{y(0)} + y(z)] + x[\overline{y(z)} + y(z)]\}}} \end{aligned}$$

# Uniform-Tree Network

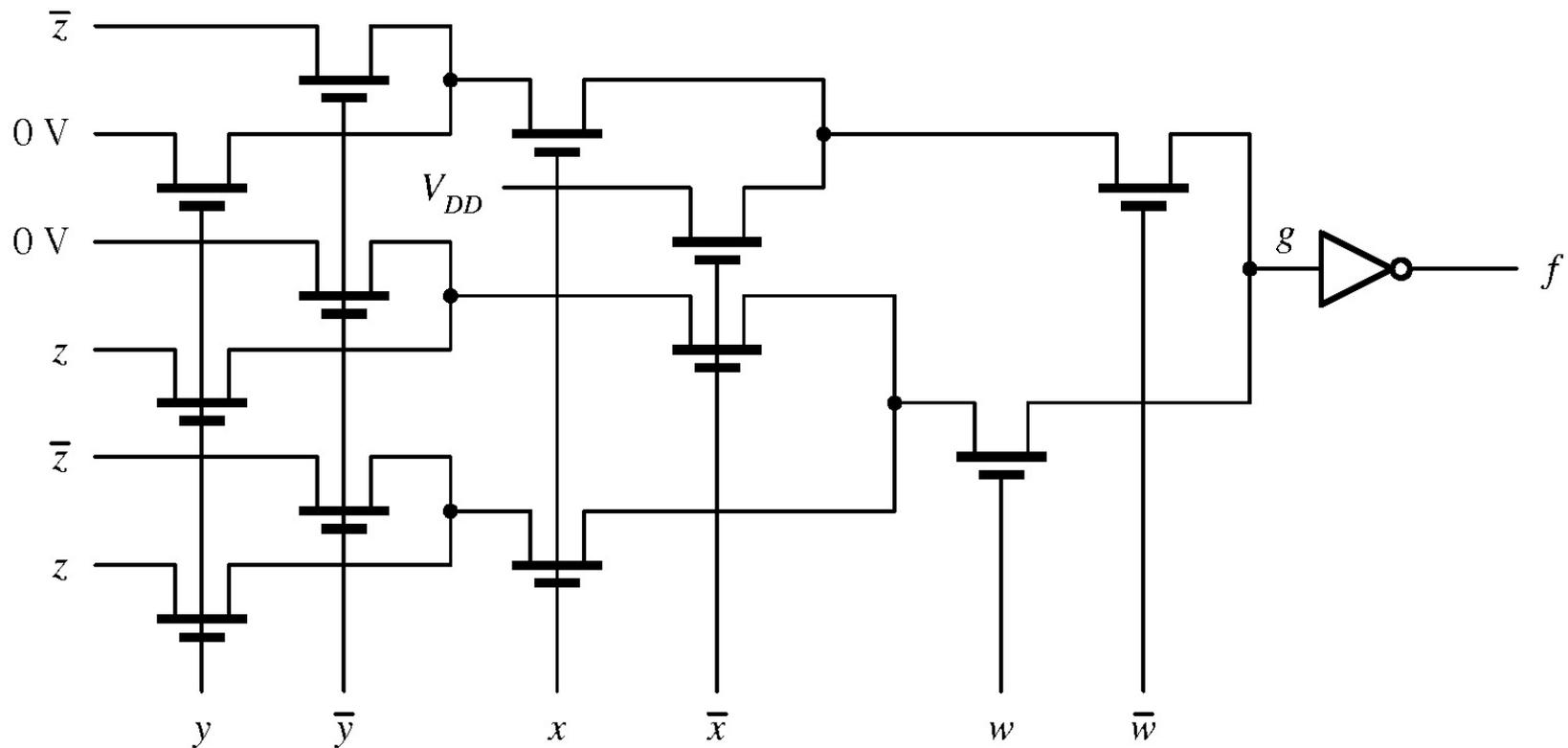

## Syllabus

- Basic operations of switches
- Switch logic circuits
- Systematic design methodologies
  - Tree network
  - $0/1-x/x'$ -tree network
  - $0/1$ -tree network

## 0/1- $x/x'$ -Tree Networks

### ■ 0/1- $x/x'$ network

- Apply Shannon's expansion theorem
- Literals  $x$ ,  $x'$  and/or constants 0/1

### ■ Constraints:


$$f_Y^0 \cup f_Y^1 \cup f_Y^x \cup f_Y^{\bar{x}} = 1$$

$$f_Y^0 \cap f_Y^1 \cap f_Y^x \cap f_Y^{\bar{x}} = \varnothing$$

$f_Y^s$  is the set of any combinations of  $Y$  such that  $R_Y(X) = s$ ,  
where  $s \in \{0, 1, x, x'\}$

# 0/1- $x/x'$ -Tree Networks

## ■ General paradigms


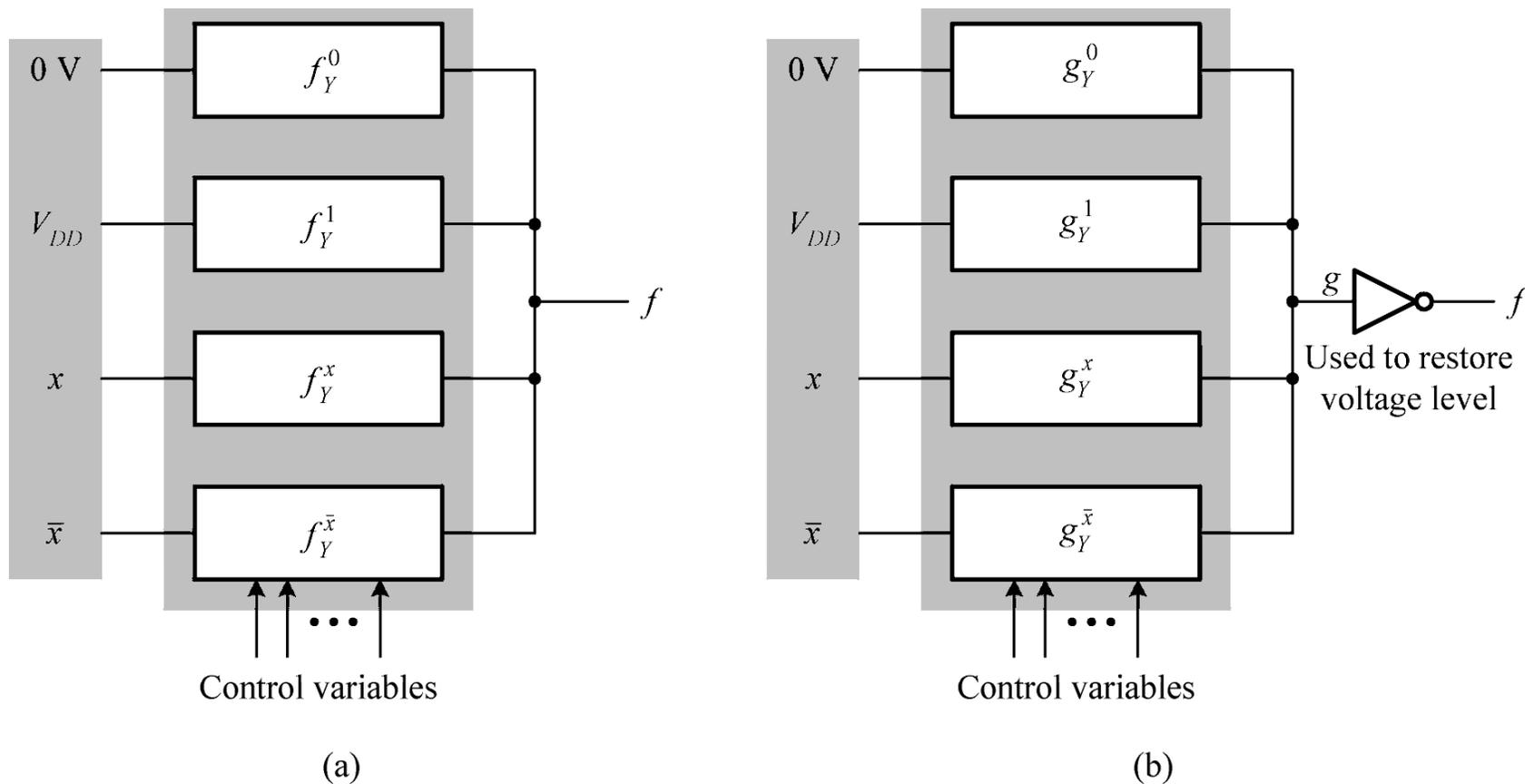


# 0/1-x/x'-Tree Network Example

- Realize the following switching function

$$f(x, y, z) = xy + xz + yz$$

	<i>yz</i>			
	00	01	10	11
<i>x</i>				
0	0	1	2	③
1	4	⑤	⑥	⑦
	↑	↑	↑	↑
	0	<i>x</i>	<i>x</i>	1

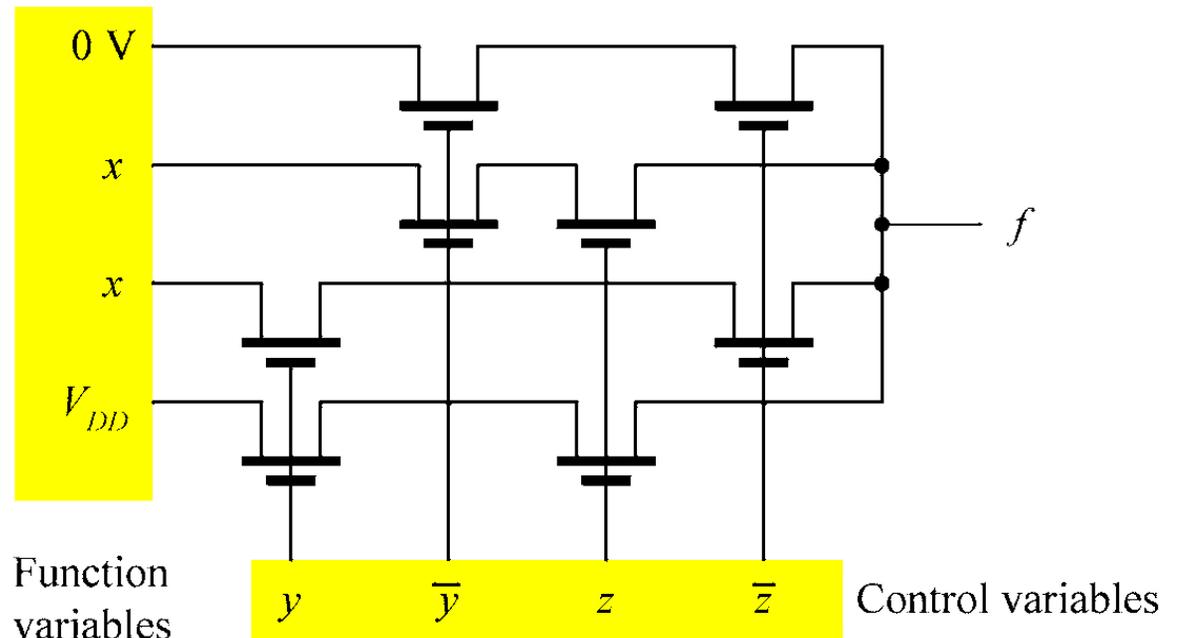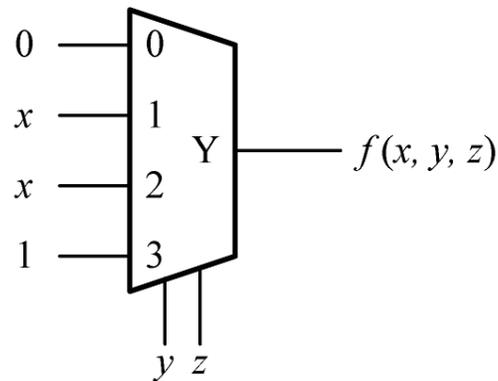

## 0/1- $x/x'$ -Tree Network Example

### ■ Example

$$f(w, x, y, z) = \overline{\overline{wx + xyz + wyz}}$$

$$g = \overline{f}(w, x, y, z) = \overline{\overline{wx + xyz + wyz}}$$

$$= \Sigma(0, 1, 2, 3, 4, 11, 12, 15)$$

$wxy$	000	001	010	011	100	101	110	111
z								
0	①	②	④	6	8	10	⑫	14
1	①	③	5	7	9	⑪	13	⑮
	↑	↑	↑	↑	↑	↑	↑	↑
	1	1	$\bar{z}$	0	0	z	$\bar{z}$	z

$$f_Y^0 = \overline{wxy} + \overline{wx\bar{y}}$$


$$f_Y^1 = \overline{wx\bar{y}} + \overline{wxy} = \overline{wx}$$

$$f_Y^z = \overline{wx\bar{y}} + \overline{wxy} = \overline{wy}$$

$$f_Y^{\bar{z}} = \overline{wx\bar{y}} + \overline{wxy} = \overline{xy}$$
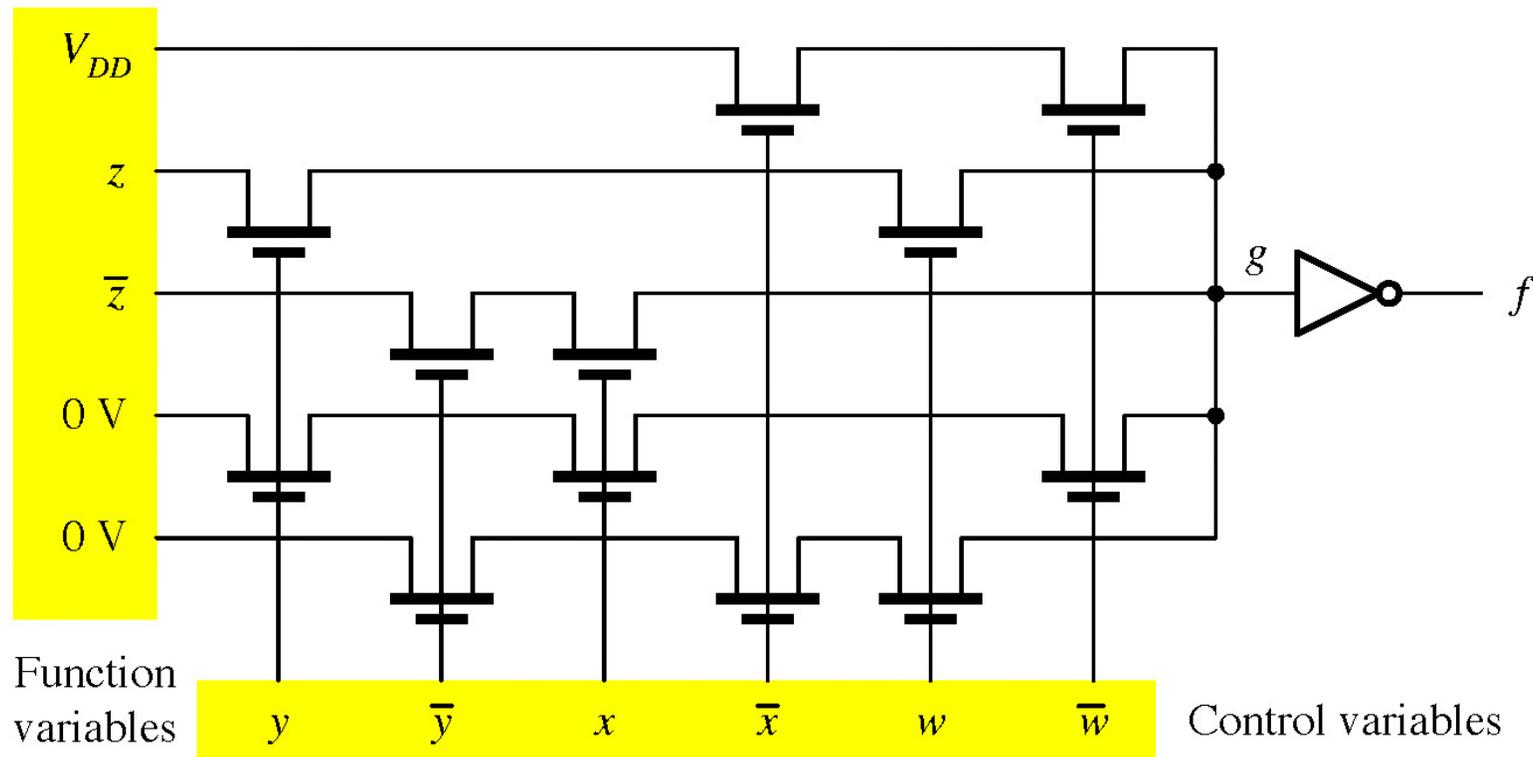
## 0/1- $x/x'$ -Tree Network Example (continued)

- The resulting logic circuit is as follows:




## Syllabus

- Basic operations of switches
- Switch logic circuits
- Systematic design methodologies
  - Tree network
  - 0/1- $x/x'$ -tree network
  - 0/1-tree network

# 0/1-Tree Networks

## ■ General paradigm

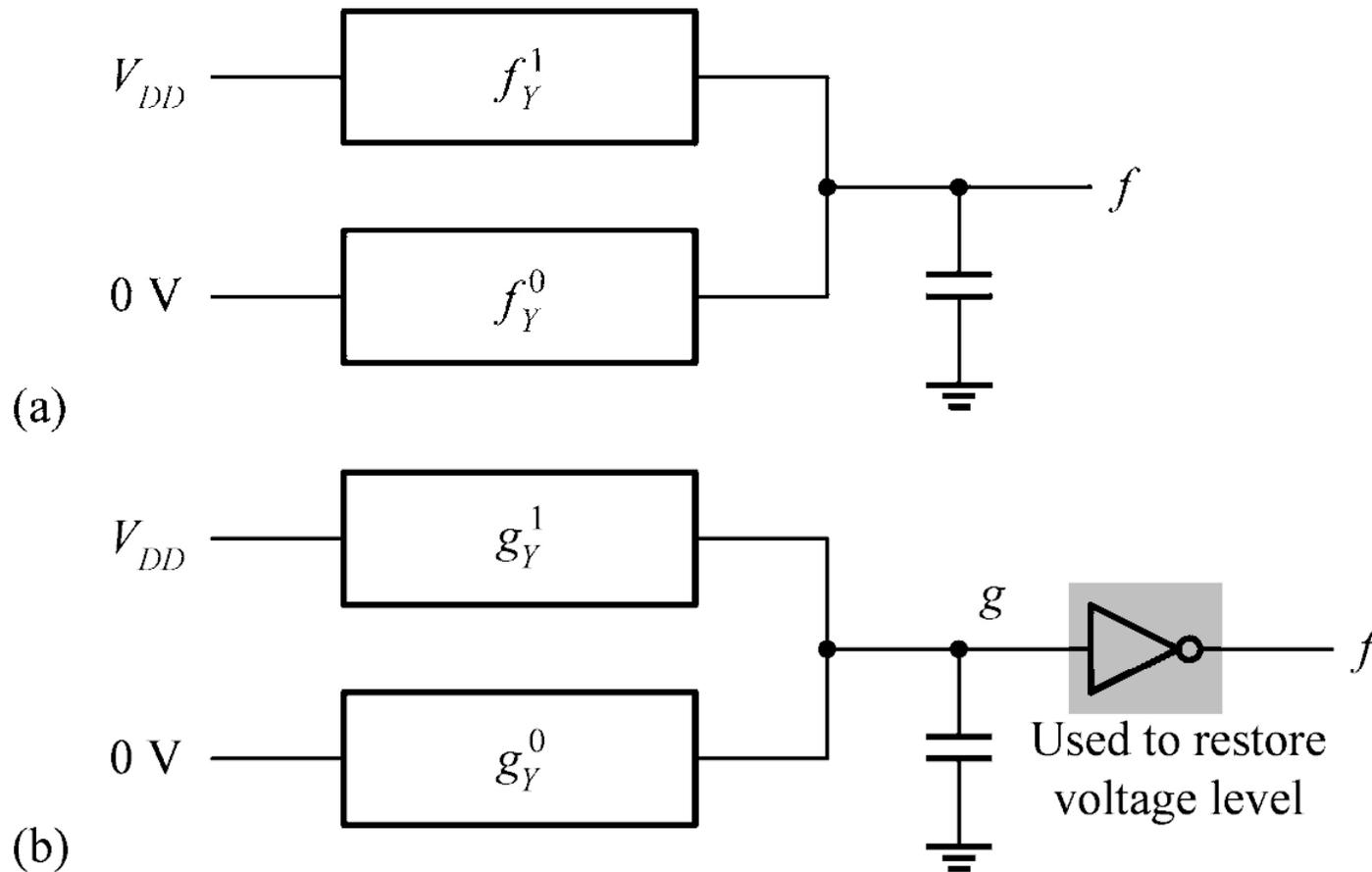


## 0/1-Tree Network Example

### ■ Example

$$f(w, x, y, z) = \overline{\overline{wx} + yz}$$


$$g(w, x, y, z) = \overline{f} = \overline{wx} + yz$$
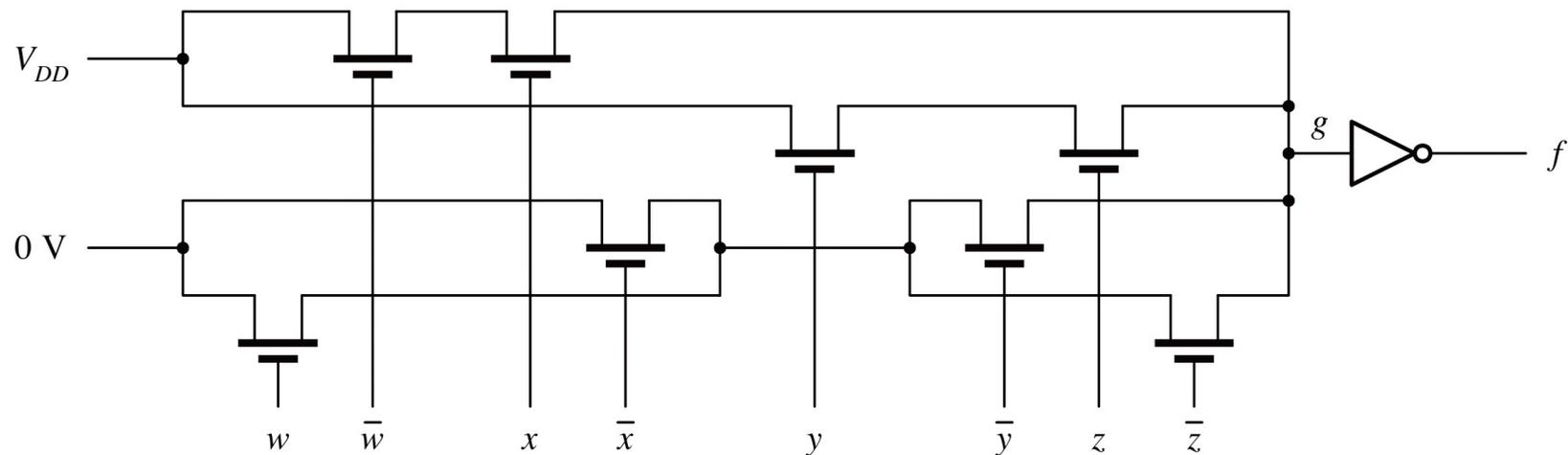
$$\overline{g} = f = \overline{\overline{wx} + yz} = (w + \overline{x})(\overline{y} + \overline{z})$$



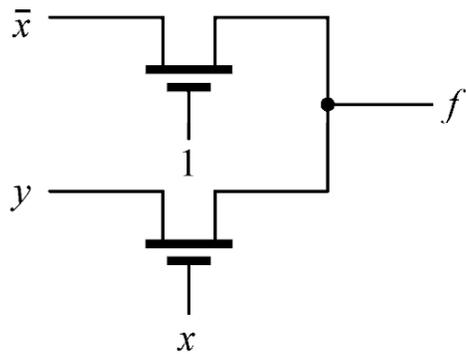
# Pitfalls of Shannon's Expansion

$$f(x, y) = \bar{x} + y = \bar{x} \cdot 1 + x \cdot y$$




$x$	$y$	$f$
0	0	1
0	1	1
1	0	0
1	1	-

(a)

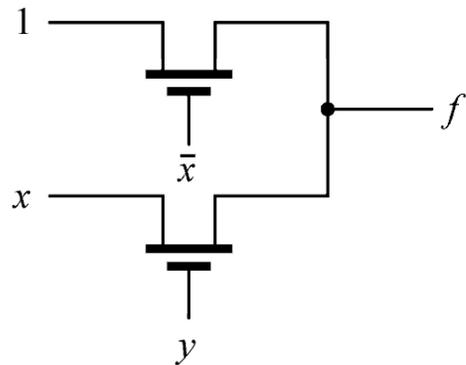

$x$	$y$	$f$
0	0	1
0	1	-
1	0	-
1	1	1

(b)

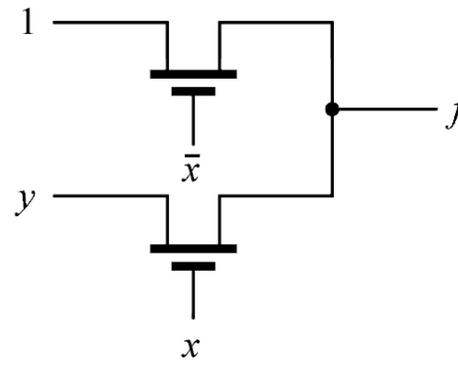

$x$	$y$	$f$
0	0	1
0	1	1
1	0	0
1	1	1

(c)