

CHAPTER 2

2.1 (c)

$$\begin{aligned}\bar{S}_{12} &= \bar{V}_1 \left(\frac{\bar{V}_1^* - \bar{V}_2}{\bar{Z}^*} \right) = (7560/\underline{10}^\circ) \left(\frac{7560/\underline{-10}^\circ - 7200/\underline{0}^\circ}{50/\underline{-90}^\circ} \right) \\ &= (7560/\underline{10}^\circ) \left(\frac{1335.5/\underline{-79.4}^\circ}{50/\underline{-90}^\circ} \right) = (7560/\underline{10}^\circ) (26.71/\underline{10.58}^\circ) \\ &= 201,927.6/\underline{20.58}^\circ = 189,016.3 + j71,046.5 \text{ VA}\end{aligned}$$

$$(a) P_{12} = 189,016.3 \text{ W}$$

$$(b) Q_{12} = 71,046.5 \text{ vars}$$

2.2 (a) From Eq. (2.7),

$$P_{12} = \frac{1}{R^2 + X^2} (R|V_1|^2 - R|V_1||V_2|\cos\gamma + X|V_1||V_2|\sin\gamma)$$

where

$$Z = 50/\underline{26}^\circ = 50(\cos 26^\circ + j\sin 26^\circ) = 44.94 + j21.92 \Omega/\Phi$$

$$\begin{aligned}P_{12} &= \frac{1}{44.94^2 + 21.92^2} (44.94|7560|^2 - 44.94|7560||7200|\cos 10^\circ \\ &\quad + 21.92|7560||7200|\sin 10^\circ) = 146,658.6 \text{ W}\end{aligned}$$

(b) From Eq. (2.8),

$$\begin{aligned}Q_{12} &= \frac{1}{R^2 + X^2} (X|V_1|^2 - X|V_1||V_2|\cos\gamma - R|V_1||V_2|\sin\gamma) \\ &= \frac{1}{44.94^2 + 21.92^2} (21.92|7560|^2 - 21.92|7560||7200|\cos 10^\circ \\ &\quad - 44.94|7560||7200|\sin 10^\circ) = -138,790.8 \text{ vars}\end{aligned}$$

$$(c) \bar{S}_{12} = P_{12} + jQ_{12} = 146,658.6 - j138,790.8 \text{ VA}$$

Alternatively, from Eq. (2.4),

$$\begin{aligned} \bar{S}_{12} &= \bar{V}_1 \left(\frac{\bar{V}_1^* - \bar{V}_2^*}{\bar{Z}} \right) = (7560/\underline{10}^\circ) \left(\frac{7560/\underline{-10}^\circ - 7200/\underline{0}^\circ}{50/\underline{-26}^\circ} \right) \\ &= (7560/\underline{10}^\circ) (26.71/\underline{-53.4}^\circ) = 201,927.6/\underline{-43.4}^\circ \\ &= 146,715.5 - j138,741.9 \text{ VA} \end{aligned}$$

$$\underline{2.3} \quad (a) \quad V_{B(L-N)} = \frac{V_{B(L-L)}}{\sqrt{3}}$$

$$V_{pu(L-L)} = \frac{V_{(L-L)}}{V_{B(L-L)}} \text{ and } V_{pu(L-N)} = \frac{V_{(L-N)}}{V_{B(L-N)}}$$

$$\text{However, } V_{(L-N)} = \frac{V_{(L-L)}}{\sqrt{3}}$$

$$\text{therefore, } V_{pu(L-N)} = \frac{V_{(L-N)}}{V_{B(L-N)}} = \frac{V_{(L-L)}/\sqrt{3}}{V_{B(L-L)}/\sqrt{3}}$$

$$= \frac{V_{(L-L)}}{V_{B(L-L)}} = V_{pu(L-L)}$$

$$(b) \quad VA_{B(1\phi)} = \frac{VA_{B(3\phi)}}{3}$$

$$\text{However, } VA_{3\phi} = 3VA_{1\phi}$$

$$\text{therefore, } VA_{pu(1\phi)} = \frac{VA_{1\phi}}{VA_{B(1\phi)}} = \frac{VA_{3\phi}/3}{VA_{B(3\phi)}/3}$$

$$= VA_{pu(3\phi)}$$

$$(c) \quad Z_{B(Y)} = \frac{[V_{B(L-N)}]^2}{VA_{B(1\phi)}} = \frac{[V_{B(L-L)}/\sqrt{3}]^2}{VA_{B(3\phi)}/3} = \frac{[V_{B(L-L)}]^2}{VA_{B(3\phi)}}$$

$$\text{However, } 3Z_{B(Y)} \triangleq Z_{B(\Delta)}$$

$$\text{therefore, } Z_{pu(Y)} = Z_{pu(\Delta)}$$

2.4 (a) For 1 ϕ system,

$$Z_B = \frac{V_B}{I_B} = \frac{1000(kV_B)}{I_B} = \frac{1000(kV_B)}{kVA_B/kV_B}$$

therefore,

$$Z_B = \frac{1000(kV_B)^2}{kVA_B} = \frac{1000(kV_B)^2}{1000(MVA_B)} = \frac{(kV_B)^2}{MVA_B}$$

$$(b) \quad \text{Since } kVA_B = \sqrt{3}(kV_B)I_{B(L)}$$

$$I_{B(L)} = \frac{kVA_B}{\sqrt{3} kV_B}$$

Also, $V_{B(L-L)} = \sqrt{3} I_{B(L)} Z_{B(3\phi)}$ from which

$$Z_{B(3\phi)} = \frac{V_{B(L-L)}}{\sqrt{3} I_{B(L)}}$$

or

$$Z_{B(3\phi)} = \frac{1000[kV_{B(L-L)}]}{\sqrt{3} I_{B(L)}} = \frac{1000[kV_{B(L-L)}]}{kVA_{B(3\phi)}/kV_{B(L-L)}}$$

$$\begin{aligned}
&= \frac{1000[kV_{B(L-L)}]^2}{kVA_{B(3\Phi)}} = \frac{1000[kV_{B(L-L)}]^2}{1000[MVA_{B(3\Phi)}]} \\
&= \frac{[kV_{B(L-L)}]^2}{MVA_{B(3\Phi)}}
\end{aligned}$$

2.5 Since $V_{B(L-L)} = \sqrt{3} V_{B(L-N)}$ (1)

and $I_{B(\Delta/\Phi)} = \frac{1}{\sqrt{3}} I_{B(Y/\Phi)}$ (2)

dividing Eq. (1) by Eq. (2) side by side,

$$Z_{B(\Delta)} = 3Z_{B(Y)}$$

2.6 In terms of line #1,

$$X_{pu(m)1} = \frac{X_{m(\text{physical}), \Omega}}{X_B} = \frac{X_{m(\text{physical})}}{V_{B(1)}/I_{B(2)}} \quad (1)$$

Using the base current in line #2, since I_2 is the current that induces mutual voltage into line #1,

$$X_{pu(m)2} = (\text{Physical } X_m) \left[\frac{I_{B(2)}}{V_{B(1)}} \right] \quad (2)$$

Multiplying right side of Eq. (2) by $(V_{B(2)}/V_{B(2)})$,

$$X_{pu(m)1} = (\text{Physical } X_m) \left[\frac{I_{B(2)}}{I_{B(1)}} \right] \left[\frac{V_{B(2)}}{V_{B(2)}} \right]$$

or

$$X_{pu(m)} = (\text{Physical } X_m) \frac{VA_B}{[V_{B(1)}][V_{B(2)}]}$$

$$\text{since } VA_B = VA_{B(1)} = VA_{B(2)}$$

$$= V_{B(1)} I_{B(1)} = V_{B(2)} I_{B(2)}$$

$$\text{Therefore, } X_{pu(m)} = (\text{Physical } X_m) \frac{MVA_B}{[kV_{B(1)}][kV_{B(2)}]}$$

2.7 (a)

$$34.5 \text{ kV}$$

$$(b) \quad Z_{B(LV)} = \frac{[kV_{B(LV)}]^2}{MVA_B} = \frac{34.5^2}{20} = 59.5125 \Omega$$

$$(c) \quad n = \frac{345/\sqrt{3}}{34.5/\sqrt{3}} = 10$$

$$(d) \quad X_{LV} = \frac{X_{HV}}{n^2} = \frac{714.15 \Omega}{10^2} = 7.1415 \Omega$$

$$(e) \quad X_{pu} = \frac{X_{LV}}{X_{B(LV)}} = \frac{7.1415}{59.5125} = 0.12 \text{ pu}$$

$$2.8 \quad (a) \quad \bar{I} = \frac{\bar{V}}{R_s + jX_s} \text{ from which } \bar{I}^* = \frac{\bar{V}^*}{R_s - jX_s}$$

$$\text{therefore, } P + jQ = \bar{V}\bar{I}^* = \frac{\bar{V}\bar{V}^*}{R_s - jX_s}$$

$$= \frac{|V|^2}{R_s - jX_s} \quad (1)$$

Multiplying Eq. (1) by its conjugate,

$$P^2 + Q^2 = \frac{|V|^4}{R_s^2 + X_s^2} \quad \text{from which}$$

$$R_s^2 + X_s^2 = \frac{|V|^4}{P^2 + Q^2}$$

From Eq. (1),

$$\begin{aligned} P + jQ &= \frac{|V|^2}{R_s - jX_s} \left(\frac{R_s + jX_s}{R_s + jX_s} \right) = \frac{|V|^2 (R_s + jX_s)}{R_s^2 + X_s^2} \\ &= \frac{P^2 + Q^2 (R_s + jX_s)}{|V|^2} \end{aligned}$$

$$\text{or } R_s + jX_s = \frac{|V|^2}{P^2 + Q^2} (P + jQ)$$

$$\text{therefore, } R_s = \frac{|V|^2}{P^2 + Q^2} (P)$$

$$(b) \text{ Thus, } X_s = \frac{|V|^2}{P^2 + Q^2} (Q)$$

$$(c) \text{ Since } Z_{pu} = (Z_{\text{physical}}) \frac{S_B}{V_B^2} \text{ pu}$$

$$R_{pu(s)} = (P_{\text{physical}}) \frac{S_B (V_{pu})^2}{P^2 + Q^2} \text{ pu}$$

$$(d) \text{ Therefore, } X_{pu(s)} = (Q_{\text{physical}}) \frac{S_B (V_{pu})^2}{P^2 + Q^2} \text{ pu}$$

2.9 (a) Since the real power absorbed depends upon the applied voltage,

$$P = \frac{V^2}{R_P} \quad \text{from which } R_P = \frac{V^2}{P}$$

$$\text{Since } Z_{pu} = (Z_{\text{physical}}) \frac{S_B}{V_B^2} \text{ pu}$$

$$R_{P(pu)} = \left(\frac{S_B}{P}\right) \left(\frac{V}{V_B}\right)^2 = \frac{V_{pu}^2}{P_{pu}} \text{ pu}$$

$$(b) \text{ Similarly } Q = \frac{V^2}{X_P} \text{ from which } X_{pu} = \frac{V^2}{Q}$$

$$\text{Therefore, } X_{P(pu)} = \left(\frac{S_B}{Q}\right) \left(\frac{V}{V_B}\right)^2 = \frac{V_{pu}^2}{Q_{pu}} \text{ pu}$$

2.10 (a) Nominally 69 kV Circuits:

$$I_{B(L)} = \frac{kVA_{B(3\phi)}}{3kV_{B(L-N)}} = \frac{5000}{3 \times 39.84} = 41.8 \text{ A}$$

$$I_{B(\phi)} = \frac{I_{B(L)}}{\sqrt{3}} = \frac{41.8}{\sqrt{3}} = 24.1 \text{ A}$$

$$Z_B = \frac{kV_{B(L-N)}}{I_{B(L)}} = \frac{39.84 \times 10^3}{41.8} = 954 \text{ } \Omega$$

$$Y_B = \frac{1}{Z_B} = \frac{1}{954} = 0.00105 \text{ S}$$

Nominally 13 kV Circuits:

$$I_{B(L)} = \frac{5000}{3 \times 7.97} = 209 \text{ A}$$

$$I_{B(\Phi)} = \frac{209}{\sqrt{3}} = 121 \text{ A}$$

$$Z_B = \frac{7.97 \times 10^3}{209} = 38.2 \text{ } \Omega$$

$$Y_B = \frac{1}{38.2} = 0.0262 \text{ S}$$

Nominally 480 V Circuits:

$$kV_{B(L-L)} = 13.8 \left(\frac{0.480}{13.2} \right) = 0.502 \text{ kV}$$

$$kV_{B(L-N)} = \frac{0.502 \text{ kV}}{\sqrt{3}} = 0.290 \text{ kV}$$

$$I_{B(L)} = \frac{5000}{3 \times 0.290} = 5750 \text{ A}$$

$$I_{B(\Phi)} = \frac{5750}{\sqrt{3}} = 3320 \text{ A}$$

$$Z_B = \frac{290}{5750} = 0.0504 \text{ } \Omega$$

$$Y_B = \frac{1}{0.0504} = 19.83 \text{ S}$$

Table P 2.10 Table for Problem 2.10

Quantity	Nominally 69kV Circuits	Nominally 13kV Circuits	Nominally 480V Circuits
$kVA_B(3\phi)$	5,000 kVA	5,000 kVA	5,000 kVA
$kV_{B(L-L)}$	69 kV	13.8 kV	0.502 kV
$kV_{B(L-N)}$	39.84 kV	7.97 kV	0.290 kV
$I_{B(L)}$	41.8 A	209 A	5760 A
$I_{B(\phi)}$	24.1 A	121 A	3320 A
Z_B	954 Ω	38.2 Ω	0.0504 Ω
Y_B	0.00105 S	0.0262 S	19.83 S

(b) Transformer T_1 :

$$\text{Rating} = 15,000 \text{ kVA} = \frac{15,000}{5,000} = 3 \text{ pu}$$

$$Z_{T_1} = 0.01 + j0.08 \text{ pu based on its ratings}$$

$$= (0.01 + j0.08) \left(\frac{5,000}{15,000} \right) \left(\frac{13.8}{13.8} \right)^2 = 0.0033 + j0.0267 \text{ pu}$$

Transformer T_2 :

$$\text{Rating} = 1,500 \text{ kVA} = \frac{1,500}{5,000} = 0.3 \text{ pu}$$

$$Z_{T_2} = 0.01 + j0.05 \text{ pu based on its ratings}$$

$$= (0.01 + j0.05) \left(\frac{5,000}{1,500} \right) \left(\frac{13.2}{13.8} \right)^2 \text{ pu}$$

$$= 0.0305 + j0.1525 \text{ pu}$$

Generator G_1 :

$$\text{Rating} = 10/12.5 \text{ MW/MVA} = \frac{12,500}{5,000} = 2.5 \text{ pu}$$

$$Z_{G_1} = j1.1 \left(\frac{5,000}{12,500} \right) \left(\frac{13.8}{13.8} \right)^2 = j0.44 \text{ pu}$$

Generator G₂:

$$\text{Rating} = 4/5 \text{ MW/MVA} = \frac{5,000}{5,000} = 1 \text{ pu}$$

$$Z_{G_2} = j0.9 \left(\frac{5,000}{5,000} \right) \left(\frac{13.2}{13.8} \right)^2 = j0.8235 \text{ pu}$$

Load 1:

$$8,000 + j6,000 \text{ kW/kvar} = \frac{8,000}{5,000} + j \frac{6,000}{5,000} = 1.6 + j1.2 \text{ pu}$$

Load 5:

$$\bar{I}_1 = |I_1|(\cos\theta + j\sin\theta) = 52.3(0.707 + j0.707)$$

$$= \frac{37 + j37}{209} = 0.177 + j0.177 \text{ pu}$$

Since it is not being solved for the circuit, assume that $V_5 = 1.0 \text{ pu}$

69 kV Circuit:

$$Z = R + jX = 50(0.445 + j0.976) \Omega$$

$$= \frac{1}{954} [50(0.445 + j0.976)] = 0.0222 + j0.0512 \text{ pu}$$


$$\frac{B}{2} = \frac{1}{2}(50)(5.78 \times 10^{-6} \text{ S}) = \frac{25 \times 5.78 \times 10^{-6} \text{ S}}{0.00105 \text{ S}}$$

$$= 0.1378 \text{ pu}$$

13 kV Circuit:

$$Z = R + jX = 2(0.8 + j0.8)$$
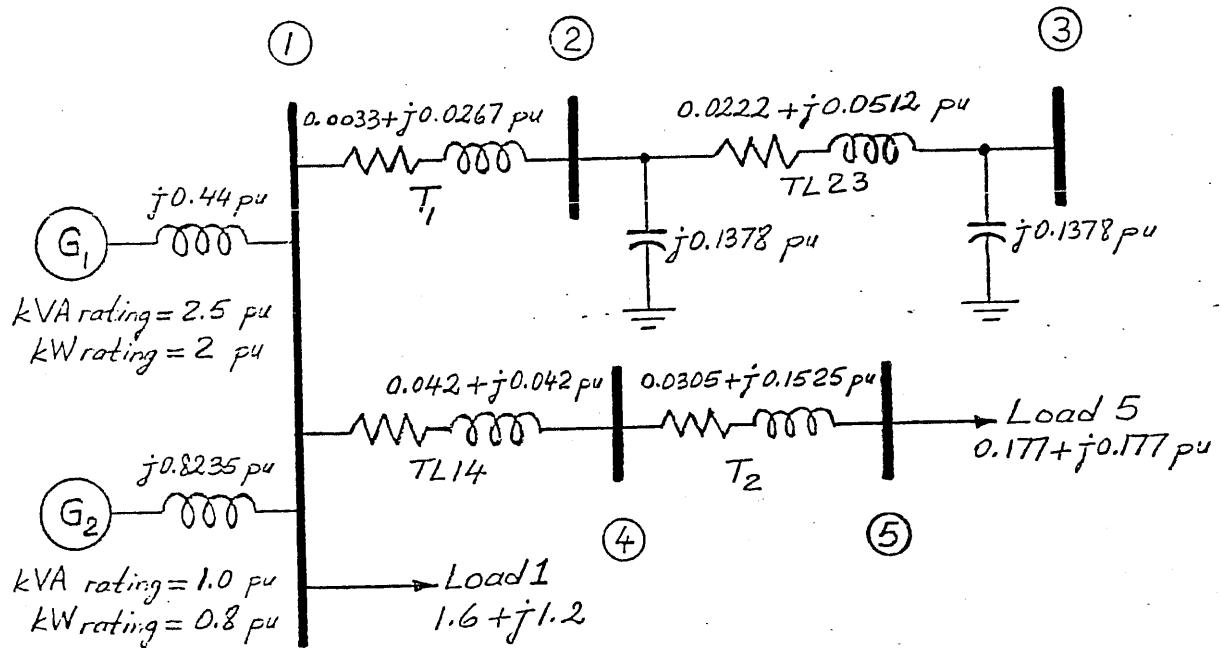
$$= \frac{1}{38.2} [2(0.8 + j0.8)] = 0.042 + j0.042 \text{ pu}$$



$$2.11 \text{ (a)} \quad S_{\text{load, pu}} = \frac{500}{1000} + j \frac{200}{1000} = 0.5 + j0.2 \text{ pu}$$

$$\text{where } P_{\text{pu}} = 0.5 \text{ pu and } Q_{\text{pu}} = 0.2 \text{ pu}$$

$$\text{Therefore, } R_{\text{pu}} = \frac{V_{\text{pu}}^2}{P_{\text{pu}}} = \frac{1.0^2}{0.5} = 2 \text{ pu}$$

$$X_{pu} = \frac{V_{pu}^2}{Q_{pu}} = \frac{1.0^2}{0.2} = 5 \text{ pu}$$

$$(b) \quad R_{pu} = \frac{V_{pu}^2 \cdot S_B \cdot P}{P^2 + Q^2} = \frac{1.0^2(1000)500}{500^2 + 200^2} = 1.7241 \text{ pu}$$

$$X_{pu} = \frac{V_{pu}^2 \cdot S_B \cdot Q}{P^2 + Q^2} = \frac{1.0^2(1000)500}{500^2 + 200^2} = 0.6896 \text{ pu}$$