

Basic Electronics





A Sign in Penacook, New Hampshire

I, V Relations for R, L and C

(Table 4.1)

Element	Unit Symbol	$I(t)$	$V(t)$	$V_{I=\text{const}}$
Resistor	R	$V(t)/R$	$RI(t)$	RI
Capacitor	C	$CdV(t)/dt$	$(1/C)\int I(\tau)d\tau$	It/C
Inductor	L	$(1/L)\int V(\tau)d\tau$	$LdI(t)/dt$	0


R, L and C Combinations

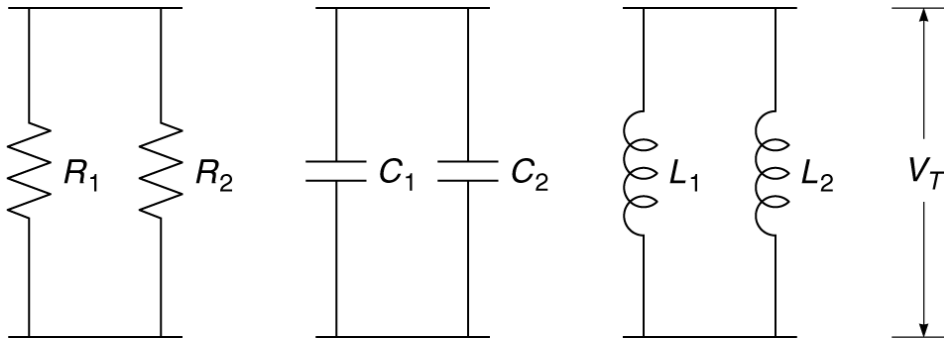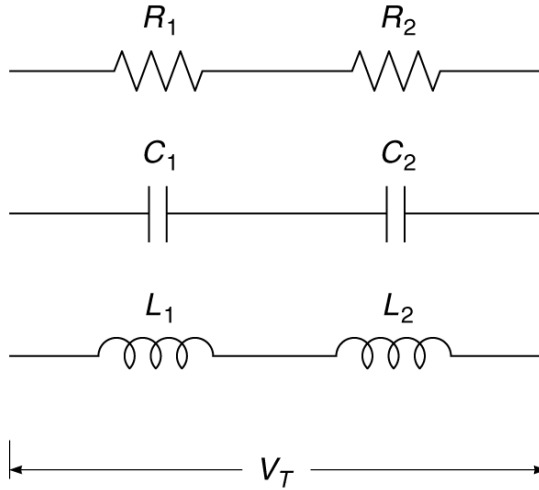

Figures 4.5 and 4.6

Basic Electronics – R, C and L

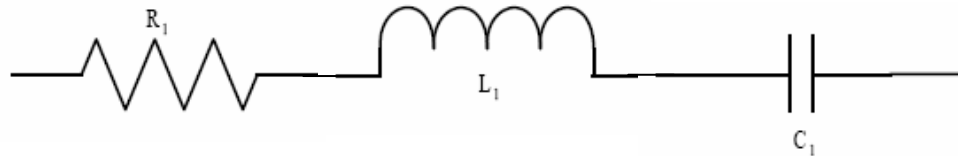- For R, C, and L combination in *series*:




Potential Difference:

Current:

- For R, C, and L combination in *parallel*:

Potential Difference:

Current:

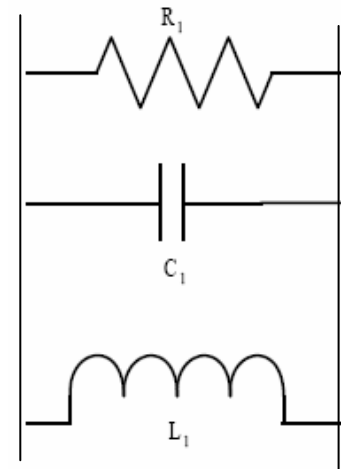

Basic Electronics – R, C and L

Current related to charge

DC: direct current →

AC: alternating current →

Determine the DC potential difference across
2 inductors in parallel:

7/31/82



Late at night, and without permission, Reuben
would often enter the nursery and conduct
experiments in static electricity.

Kirchhoff's Laws

Node: a point in a circuit where any two or more elements meet


Loop: a closed path going from one circuit node back to itself without passing through any intermediate node more than once


Kirchhoff's first (or current) law: at a circuit node, the current flowing into the node equals the current flowing out (charge is conserved)

Kirchhoff's second (or voltage) law: around a circuit loop, the sum of the voltages equal zero (energy is conserved)

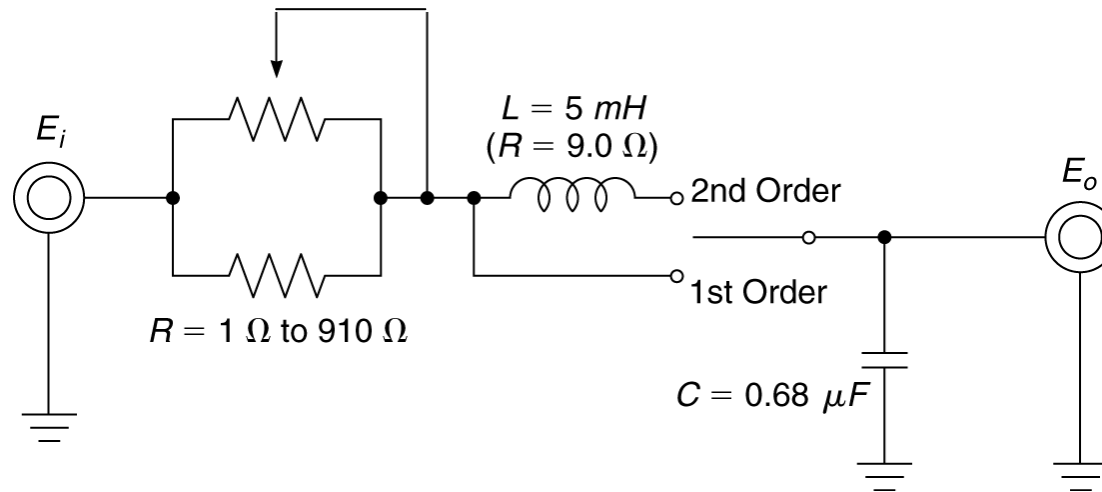Example RLC Circuit


- Consider a RLC circuit used in your 'Dynamic System Response' laboratory exercise.



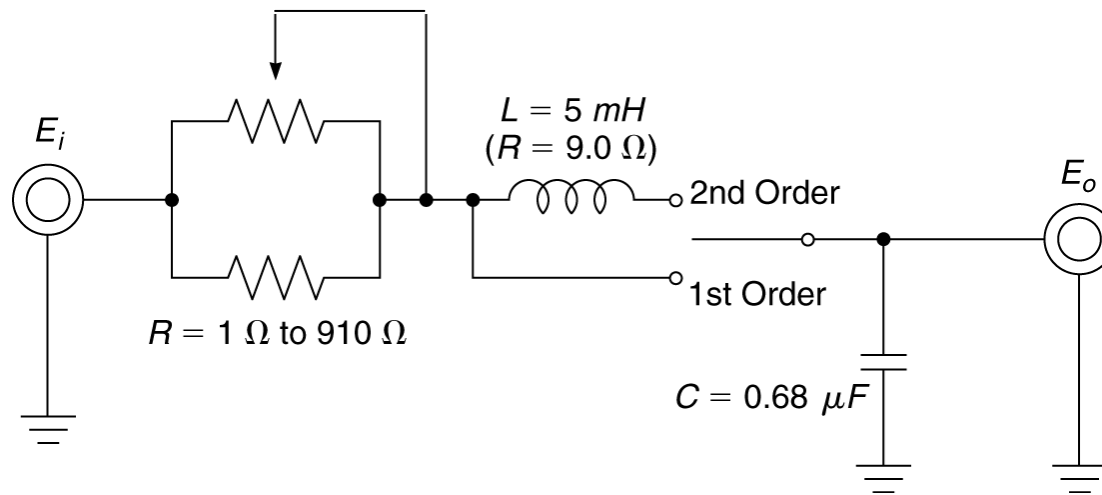

- E_i , R , L and C are in series \rightarrow

- Recall that $I = dQ/dt \rightarrow$

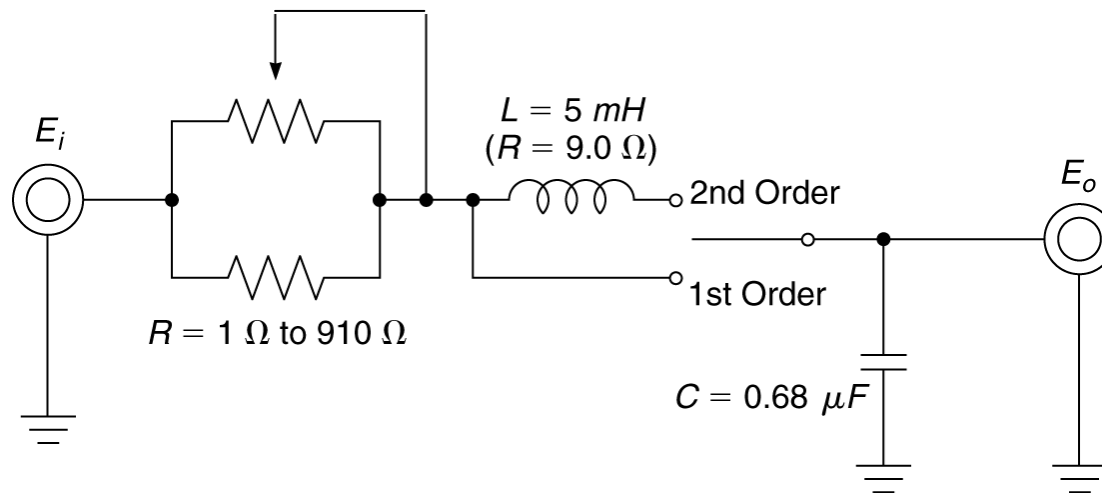

- Now examine another loop and apply Kirchoff's Voltage Law again.

The Wheatstone Bridge

Use Kirchhoff's Voltage Law:

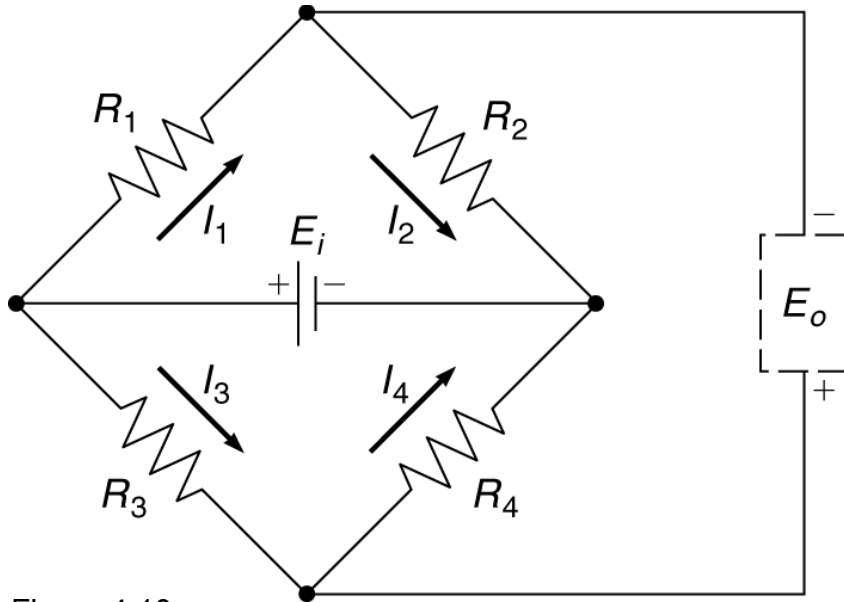


Figure 4.10

- What is the Wheatstone bridge equation if another resistor, R_x , is added in *parallel* with R_1 ?

