
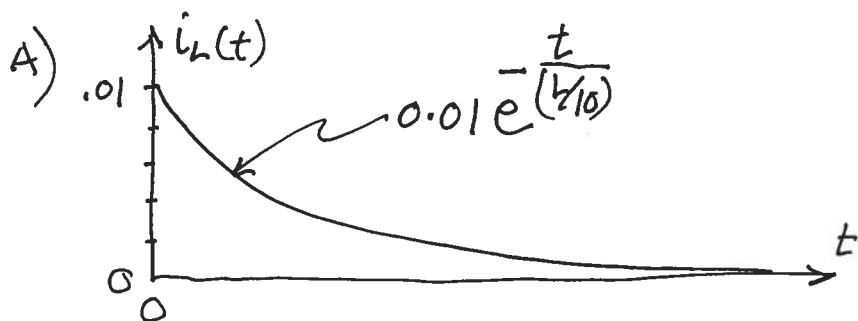


## CHAPTER 2 H.P. SOLUTIONS:

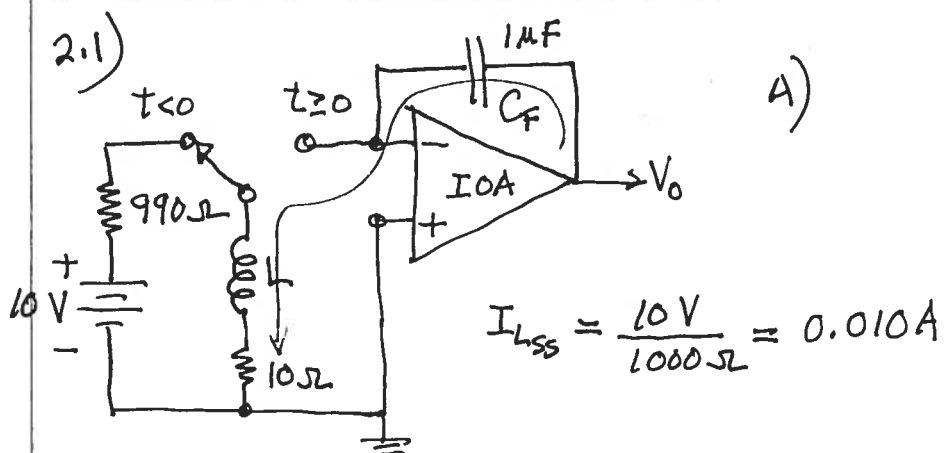


$$\int e^u du = e^u$$


B)

$$V_{o_{ss}} = V_{c_{ss}} = \frac{1}{C} \int_0^{\infty} i_L(t) dt = \frac{0.01}{10^{-6} F} \int_0^{\infty} e^{-\frac{t}{10}} dt$$
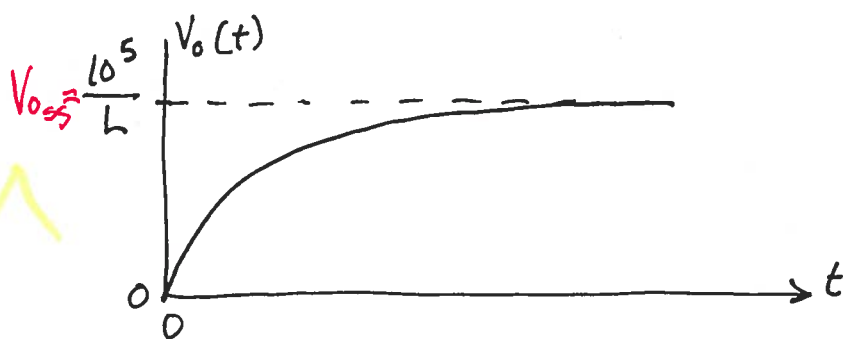
$$V_{o_{ss}} = 10^4 \left( -\frac{10}{L} \right) [0 - 1] = \frac{10^5}{L}$$



2.2)

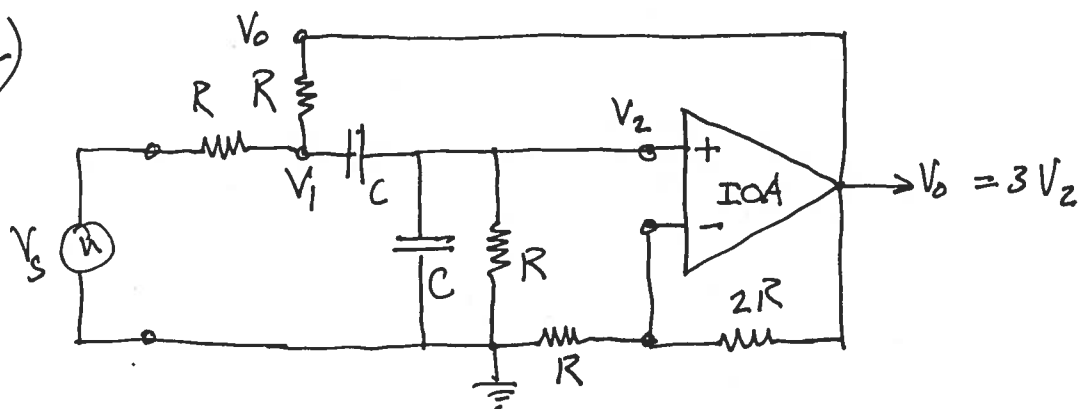

A) FIND  $\frac{V_o}{V_s}(s)$ : WRITE 2 NODE EQUATIONS:

USE CRAMER'S  
RULE

$$\begin{cases} V_1[2G + sC] - 3V_2G - V_2sC = V_sG \\ -V_1sC + V_2[G + 2sC] = 0 \end{cases}$$

$$\Delta = \begin{vmatrix} [2G + sC] & -[3G + sC] \\ -sC & [G + 2sC] \end{vmatrix} = 2G^2 + s2GC + s^2C^2$$

$$\Delta V_2 = \begin{vmatrix} (2G + sC) & V_sG \\ -sC & 0 \end{vmatrix} = V_s s C G$$

A)

$$\frac{V_o}{V_s}(s) = \frac{s \frac{3CR}{2}}{\left(s^2 \frac{R^2 C^2}{2} + sRC + 1\right)}$$

B)  $\omega_n = \frac{\sqrt{2}}{RC} \text{ r/s}, \frac{2\zeta}{\omega_n} = RC \rightarrow \zeta = \frac{\omega_n RC}{2} = \frac{\sqrt{2} RC}{2RC} = \frac{\sqrt{2}}{2} = \underline{\underline{0.7071}}$


& PK GAIN @  $\omega = \omega_n$

$$\frac{V_o}{V_s}(j\omega_n) = \frac{j\omega_n \frac{3CR}{2}}{j\omega_n RC} = \frac{3}{2} = \underline{\underline{1.5}}$$

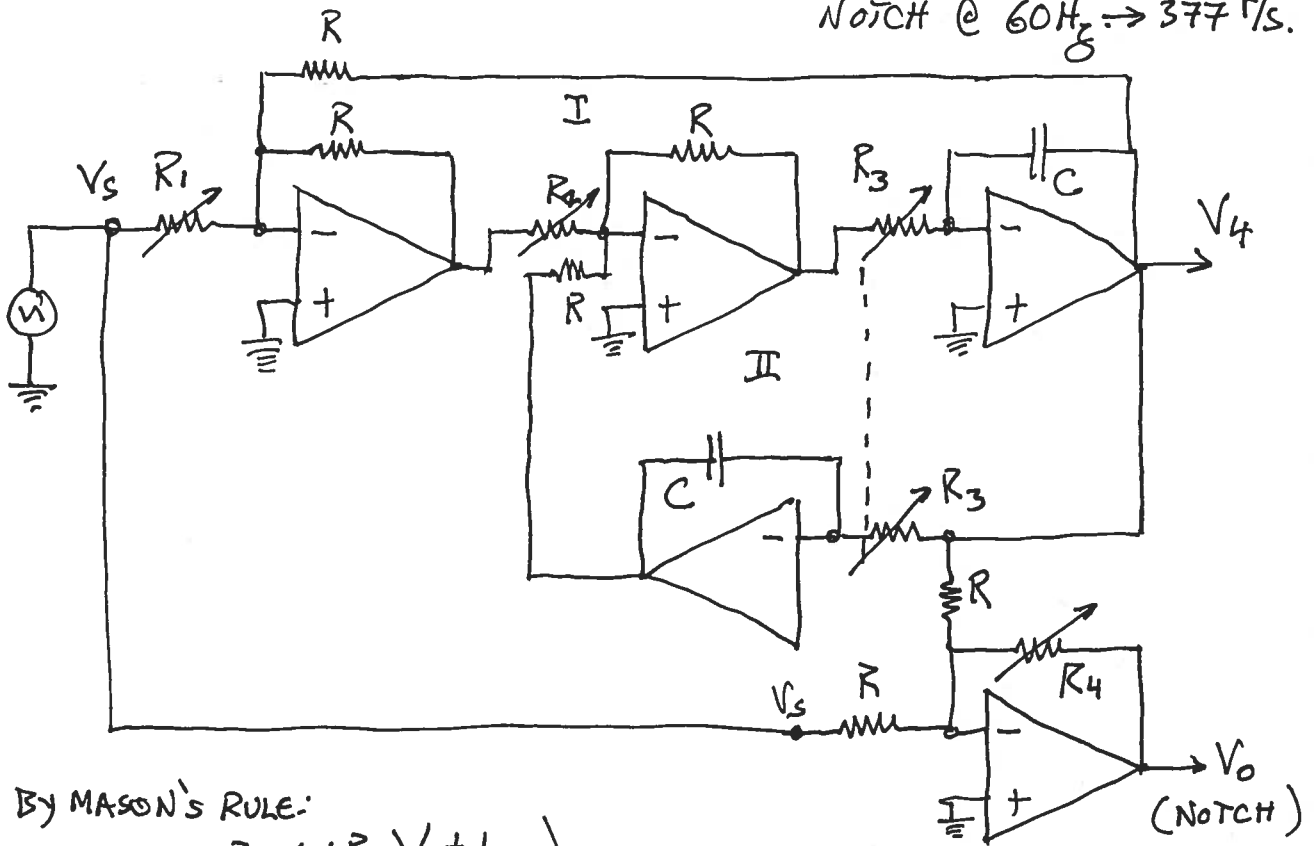2.3) 2-LOOP, BIQUAD NOTCH FILTER: HAS  $Q = 50$ ,  $A_{v0} = 20dB$  or  $\times 10$

$$f_b = > 100 \text{ kHz}$$

$$\text{NOTCH @ } 60 \text{ Hz} \rightarrow 377 \text{ r/s.}$$



By MASON'S RULE:

$$\frac{V_4}{V_s} = \frac{\left(\frac{-R}{R_1}\right) \left(\frac{+R}{R_2}\right) \left(\frac{+1}{s R_3 C}\right)}{1 + \left[ \underbrace{(+1) \left(\frac{+R}{R_2}\right) \left(\frac{+1}{s R_3 C}\right)}_{\text{LOOP I}} + \underbrace{(+1) \left(\frac{+1}{s R_3 C}\right) \left(\frac{+1}{s R_3 C}\right)}_{\text{LOOP II}} \right] + 0}$$

(NO NONTOUCHING LOOPS)

$$= \frac{-s R_3 C R^2 / R_1 R_2}{s^2 (R_3 C)^2 + s (R_3 C) \frac{R}{R_2} + 1} \quad (\text{BPF}) \quad \omega_n = \frac{1}{R_3 C} \text{ r/s}$$

$$\frac{2\zeta}{\omega_n} = \frac{R_3 C R}{R_2} = \frac{1}{Q \omega_n}$$

$$\therefore \downarrow Q = \frac{R_2}{R} \approx 50, \therefore R_2 = 50R$$

$$V_0 = \left(\frac{-R_4}{R}\right) [V_s + V_4]$$

$$\downarrow$$

$$\frac{V_0(s)}{V_s} = \left(\frac{-R_4}{R}\right) \left[ 1 - \frac{s \frac{R^2}{R_1 R_2} R_3 C}{[s^2 (R_3 C)^2 + s R_3 C \frac{R}{R_2} + 1]} \right] \rightarrow$$

2.3) CONT'D.

$$\frac{V_o}{V_s}(s) = -\frac{R_4}{R} \left\{ \frac{s^2(C_3 R)^2 + s(R_3 C) \frac{R}{R_2} + 1 - \frac{R^2}{R_1 R_2} s(R_3 C)}{s^2(C_3 R)^2 + s \frac{R}{R_2} C_3 R + 1} \right\}$$

\* TO MAKE NUMERATOR  $s^1$  TERM VANISH

$$\frac{1}{R_2} R = \frac{R^2}{R_1 R_2} \rightarrow \text{MAKE } R = R_1$$

NOW:

$$\frac{V_o}{V_s}(s) = \frac{(s^2(R_3 C)^2 + 1)}{(s^2(R_3 C)^2 + s(R_3 C) \frac{R}{R_2} + 1)}$$

\* DESIGN:

$$* \text{SET } C = 1 \mu\text{F} = 10^{-6} \text{ F}$$

$$\omega_n = \frac{1}{R_3 \times 10^{-6}} = 2\pi 60 = 377$$


$$R_3 = 2.653 \text{ E}3 \Omega \text{ FOR } 60 \text{ Hz NOTCH}$$

$$* \text{SET } R = 1 \text{ K} \Omega$$

$$\therefore R_1 = 1 \text{ K} \Omega, \quad R_2 = 50 \text{ K} \Omega, \quad R_3 = 2.653 \text{ K} \Omega$$

\* NOW DO SIM.

2.4)

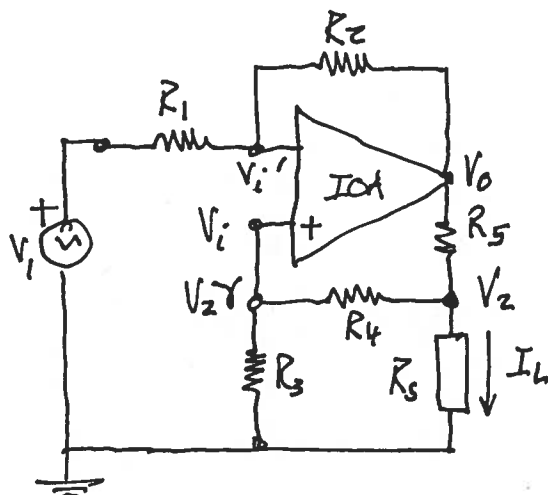

$$\alpha \equiv \frac{R_2}{R_1 + R_2}, \quad \beta \equiv \frac{R_1}{R_1 + R_2}$$

$$\gamma \equiv \frac{R_3}{R_3 + R_4}$$

FIND:

$$* G_M = \frac{I_L}{V_1}$$

\* CONDITIONS ON CKT SO  $I_L$  INDEPENDENT OF  $R_5$ 

$$* \text{AS IOA: } V_i' = V_1 \alpha + V_o \beta = V_2 \gamma$$

$$* \text{DO KCL ON } V_2 \text{ NODE: } V_2 \left[ G_5 + G_5 + \frac{1}{R_3 + R_4} \right] = V_o G_5 \Rightarrow$$

2.4) CONT'D: Now  $V_0 = \frac{\gamma V_2 - V_1 \alpha}{\beta}$ , so

$$V_2 \left[ G_S + G_5 + \frac{1}{R_3 + R_4} \right] = G_5 \left[ \frac{\gamma V_2 - \alpha V_1}{\beta} \right]$$

↓ (ALG)

$$V_2 \left[ G_S R_5 + \left( 1 + \frac{R_5}{R_3 + R_4} - \frac{\gamma}{\beta} \right) \right] = -V_1 \frac{\alpha}{\beta}$$

MAKE  $\rightarrow 0$  ↗

$$\frac{R_2}{R_1} = \frac{\alpha}{\beta}$$

$$\downarrow$$

$$V_2 [G_S R_5] = -V_1 \frac{\alpha}{\beta} \rightarrow V_2 = \frac{-V_1 \alpha / \beta}{G_S R_5}$$

$$\text{Now } \boxed{I_L = \frac{V_2}{R_5} = \frac{-V_1 \alpha / \beta}{R_5 G_S R_5} = -V_1 \frac{R_2}{R_1 R_5}, \therefore G_M = -\frac{R_2}{R_1 R_5} S}$$

TO MAKE (\*)  $\rightarrow 0$ ;

$$\frac{R_5 R_3}{R_3 (R_3 + R_4)} = \frac{\gamma}{\beta} \rightarrow 1 = \frac{\overset{R_3 \checkmark \gamma}{R_3 + R_4}}{\underset{R_1 + R_2 \leftarrow \beta}{R_1}} - 1 \rightarrow 0$$

\* AFTER MUCH ALGEBRA:

1. MAKE:  $\gamma > \beta$

2. MAKE:  $R_2 R_3 - R_1 R_4 = R_1 R_5$

$$\text{FOR } \boxed{\frac{I_L}{V_1} = -\frac{\alpha}{\beta} G_S}$$


2.5) DEBBOO NON-INVERTING INTEGRATOR:  $OA \equiv IDEAL$ ,

$$R_1 \equiv R_1', R_2 \equiv R_2'.$$

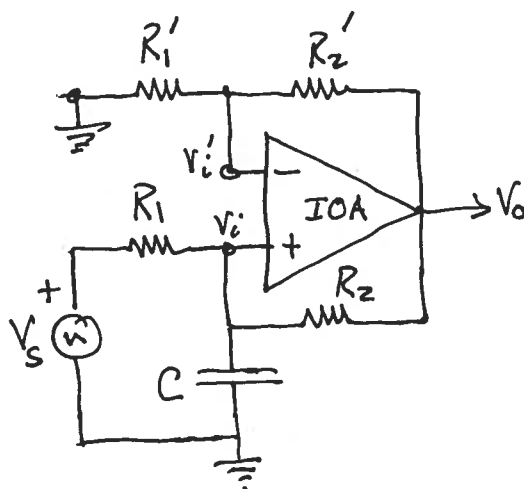A)  $\frac{V_o}{V_s}(s)$

$$\beta \equiv \frac{R_1}{R_1 + R_2}$$

$$V_i' = V_o \frac{R_1'}{R_1' + R_2'} = V_i$$



By KCL:  $V_i [G_1 + G_2 + sC] - G_2 V_o - V_s G_1 = 0$

$$\downarrow$$

$$V_o \beta [G_1 + G_2 + sC] - V_o G_2 = V_s G_1$$


$$\downarrow$$

$$\frac{V_o}{V_s} = \frac{G_1}{\beta \left[ \frac{R_2 + R_1}{R_1 R_2} + sC \right] - G_2} = \frac{G_1}{\beta \left[ \frac{G_2}{\beta} + sC \right] - G_2}$$

$$\therefore \boxed{\frac{V_o}{V_s} = \frac{G_1}{sC\beta} = \frac{1}{sCR_1\beta}}$$

B) CONSIDER BIAS CURRENTS:

$$V_s \equiv 0$$

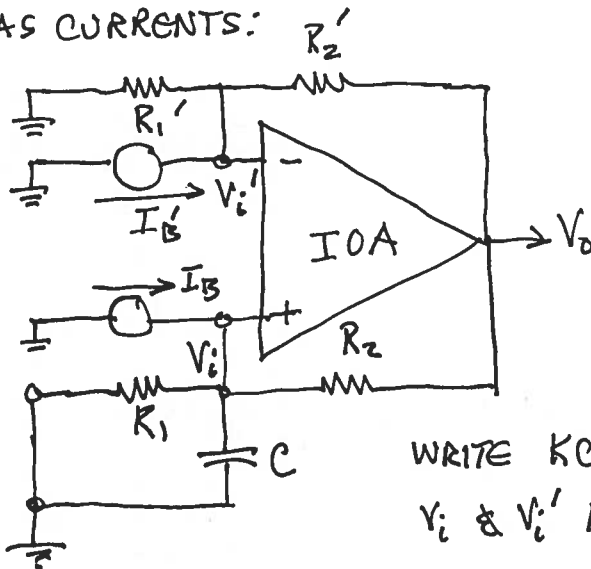

WRITE KCL NODE EQS FOR  $V_i$  &  $V_i'$  NODES.

2.5) CONT'D

$$B) \quad V_i' [G_1 + G_2] - V_o G_2 = I_B'$$

$$V_i' [sC + G_1 + G_2] - V_o G_2 = I_B, \quad V_i' = \frac{I_B' + V_o G_2}{G_1 + G_2}$$

$$\therefore \frac{I_B' + V_o G_2}{(G_1 + G_2)} [sC + (G_1 + G_2)] - V_o G_2 = I_B$$

AFTER SOME ALGEBRA:

$$V_o = (I_B - I_B') \frac{R_1 + R_2}{sC R_1} = (I_B - I_B') \frac{1}{sC \beta} - I_B' R_2$$

OFFSET CURRENT,  $I_{os}$  \*

$$\text{LET } I_B(t) = I_B u(t) \text{ \& } I_B' = I_B' u(t)$$

STEP


$$\therefore I_B(s) = \frac{I_B}{s}, \quad I_B'(s) = \frac{I_B'}{s}$$

$$\therefore V_o(s) = \frac{I_B - I_B'}{s} \frac{1}{sC \beta} - \frac{I_B'}{s} R_2$$

$\downarrow \mathcal{I}^{-1}$




$$V_o(t) = I_{os} \frac{t}{C \beta} - I_B' R_2 u(t), \quad t \geq 0$$

2.6)

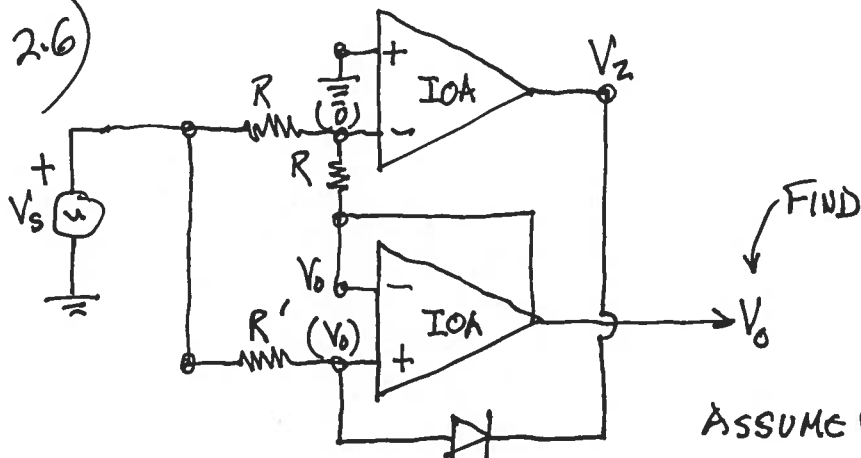

ASSUME DIODE IS IDEAL!

2.6) CONT'D.  $V_s < 0$ :

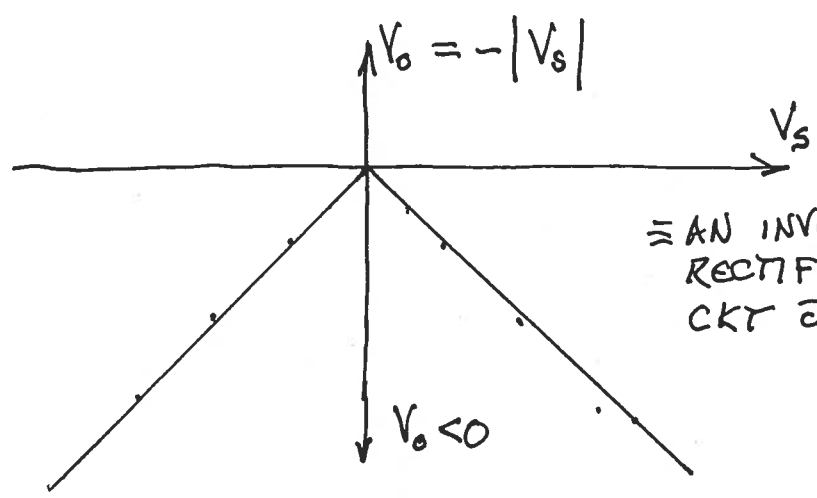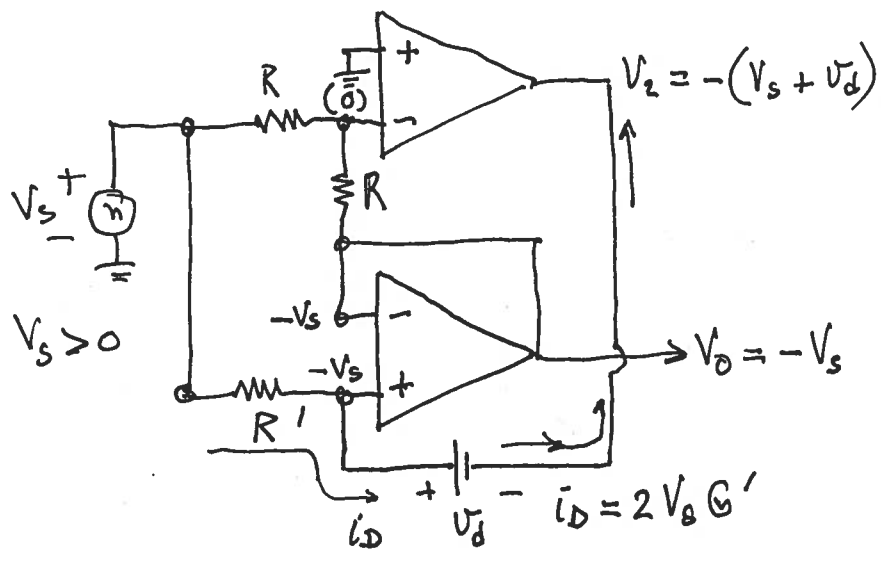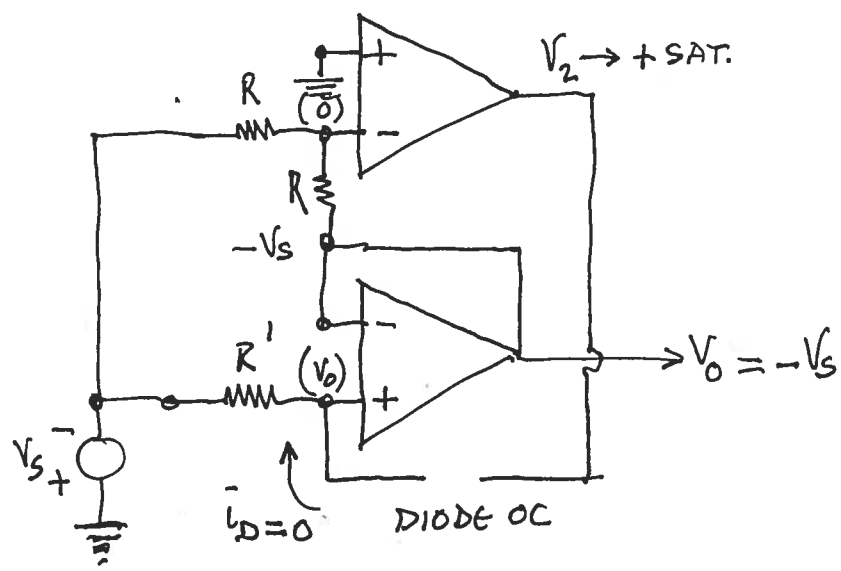

≡ AN INVERTING FULL-WAVE RECTIFIER (OR ABSVAL) CKT @ UNIT GAIN.

2.7) DESIGN 60Hz NOTCH FILTER:

$$\alpha \equiv \frac{R_2}{R_1 + R_2}$$

\* CLEARLY,  $V_2 = -3V_s$ ,  $V_3 = -3V_s \frac{R_2}{R_1 + R_2} = -3V_s \alpha$

\* USING SUPERPOSITION ON IOA-2:

$$V_o(s) = -3V_s \left[ \frac{-sCR_3}{(1+sCR_3)^2} \right] + -3V_s \alpha \left[ 1 + \frac{1}{\frac{1}{sC} + R_3} \right]$$

↓ ALGEBRA

SET  $\alpha \equiv \frac{1}{3}$

$$\frac{V_o}{V_s}(s) = \frac{-[s^2(R_3C)^2 + 1]}{[s^2(R_3C)^2 + s2R_3C + 1]} \quad \leftarrow \text{NOTCH} \quad \zeta = 1, Q = \frac{1}{2}$$

DESIGN:  $R_1 \equiv 1K$ ,  $R_2 \equiv 2K$ ,  $\therefore \alpha = \frac{1}{3}$ ,  $R_3 \equiv 10K$

$$\therefore C = \frac{1}{2\pi 60 \times 10^4} = \underline{\underline{2.653 \text{ E-7 F}}}$$


=(377)

\* DEEPEST NOTCH CA. -80 dB USING FIXED-STEP INTEG.

2 0.05% Acc.,  $Q = \frac{\omega_f}{\zeta \omega_0} \approx \frac{60}{60} = 1$

\* See NEXT PAGE FOR PLOT: OP-37 OA'S WERE USED & MICROCAP SIM.

2.7) BODE  
PLOT

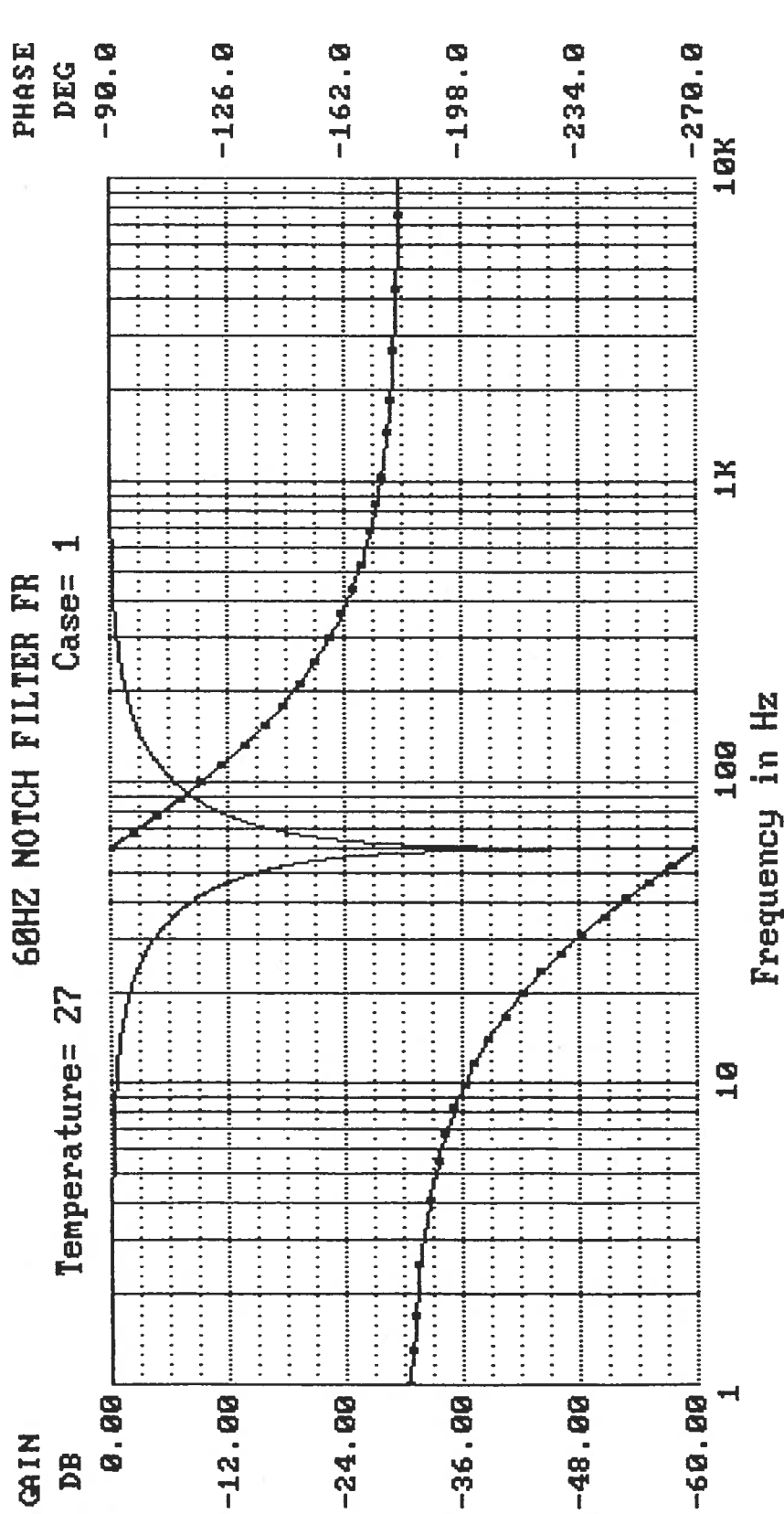

Frequency = 100.00000E+02 Hz      Gain = -.009 Db  
 Phase angle= -179.349 Degrees      Group delay= 0.00000E+00  
 Gain slope = 115.82310E-05 Db/Oct      Peak gain = -.009Db/F= 100.00000E+02


2.8) SINGLE-LOOP BIQUAD: (SEE FIG. P2.8)

A)  $\frac{V_o}{V_s}(s)$  IN TC FORM: USING MASON'S RULE:

$$\frac{V_o}{V_s}(s) = \frac{-\left(\frac{1}{sC + G_2}\right) \frac{1}{R_1}}{1 + \left[ (+1) \left( \frac{+1}{sR_3C} \right) \left( + \frac{1}{sC + G_2} \right) \frac{1}{R_3} \right]}$$

↓
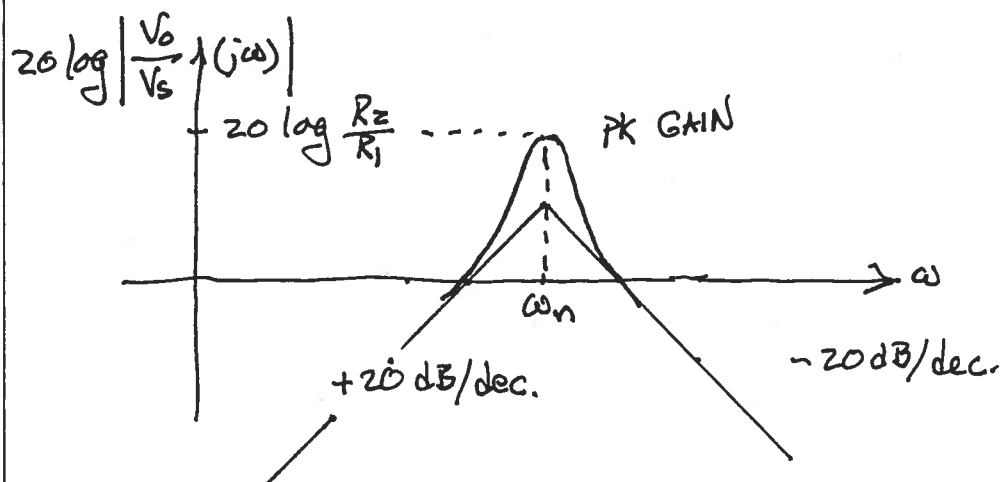
$$\frac{V_o}{V_s}(s) = \frac{-sCR_3 \left( \frac{R_3}{R_1} \right)}{s^2(CR_3)^2 + sCR_3 \left( \frac{R_3}{R_2} \right) + 1} \quad (\text{TC FORM})$$



B)  $\omega_n = \frac{1}{CR_3} \text{ r/s}, \quad \frac{2\zeta}{\omega_n} = R_3 C \frac{R_3}{R_2} \rightarrow \zeta = \frac{R_3}{2R_2}, \quad Q = \frac{1}{2\zeta} = \frac{R_2}{R_3}$

THERE IS MUCH INTERACTION BETWEEN R'S: PK GAIN @  $\omega = \omega_n$

DESIGN: 1) PICK  $\omega_n, C$ , FIND REASONABLE  $R_3$   $\approx -\frac{R_2}{R_1}$

( $1 \text{ k}\Omega \leq R_3 \leq 1 \text{ M}\Omega$ );

2) PICK  $\zeta$  (OR  $Q$ ).  $R_2$  SETS  $Q$ ;  $R_1$  SETS GAIN.

2.9) (SEE FIG P2.9)

A)  $V_o = -I_1 R_F$

B) SYSTEM WILL BE UNSTABLE:

IF OA  $K_{V_o}$  IS FINITE,  $\beta K_{V_o} < 1$

so  $\beta < \frac{1}{K_{V_o}}$ .  $V_o \cong V_i \frac{1}{\beta}$

C)  $V_o = \frac{-1}{sC} I_1$

D)  $\frac{V_o}{V_i}(s) = \frac{-\frac{1}{(G_2 + sC_2)}}{(R_1 + \frac{1}{sC_1})} = \frac{-sC_1 R_2}{(sC_2 R_2 + 1)(sC_1 R_1 + 1)}$

AMID =  $-\frac{C_1}{C_2}$

E)  $V_o(s) = -V_i(s) \frac{R_2 + \frac{1}{sC_2}}{R_1} \rightarrow \frac{V_o}{V_i}(s) = \frac{-(sC_2 R_2 + 1)}{sC_2 R_1}$

F)  $\frac{V_o}{V_i}(s) = -\frac{(sC_1 R_1 + 1)}{sC_2 R_1}$

G)  $\frac{V_o}{V_i}(s) = -\frac{sC_1 R_2}{(sC_1 R_1 + 1)}$

2.10) LINEARIZED WHEATSTONE BRIDGE: (SEE FIG P2.10)

FIND  $V_o$ : N.B:  $V_2 = V_3 \cong 0$  AS IOA.

~~$$\begin{cases} V_2 \left[ G_3 + \frac{1}{R + \Delta R} \right] - \frac{V_1}{R + \Delta R} = V_s G_3 \\ V_3 \left[ G_3 + G_1 + G_2 \right] - V_1 G_1 - V_o G_2 = V_s G_3 \end{cases}$$~~

1)  $-\frac{V_1}{R + \Delta R} = V_s G_3$ ; 2)  $-V_1 G_1 - G_2 V_o = V_s G_3 \Rightarrow$

2.10) CONT'D:

$$V_i = -V_s G_3 (R + \Delta R) \quad \begin{array}{c} \text{SUB.} \\ \downarrow \\ -V_i G_1 - V_o G_2 = V_s G_3 \end{array}$$

$$\downarrow \text{ALG}$$

$$V_o = \left( \frac{\Delta R}{R} \right) \frac{R_2}{R_3}$$

2.11) Re: CMRR

$$\text{CMRR @ } 60\text{Hz} \equiv 120\text{dB} \rightarrow 10^6 (\text{NUMERIC})$$

$$\text{CMRR} \equiv \frac{A_D}{A_C} = 10^6 \quad V_o = A_D V_{id} + A_C V_{ic} \quad (\text{D.A. OUTPUT})$$


$$V_{id} = \frac{.004 + 0}{2} = 0.002 \text{ Vpk}, \quad V_{ic} = \frac{.004 + 0}{2} = 0.002 \text{ Vpk.}$$

$$1.414_{\text{PK}} = .002 A_D + 0.002 A_C$$

$$\therefore A_D + A_C = \frac{1.414}{.002} = 707.1$$

$$\left. \begin{array}{l} \downarrow \\ (10^6 A_C + A_C) \cong 707.1 \rightarrow A_C \cong 7.071 \text{E-}4 \\ \therefore A_D \cong 707.1 \end{array} \right\}$$

2.12)

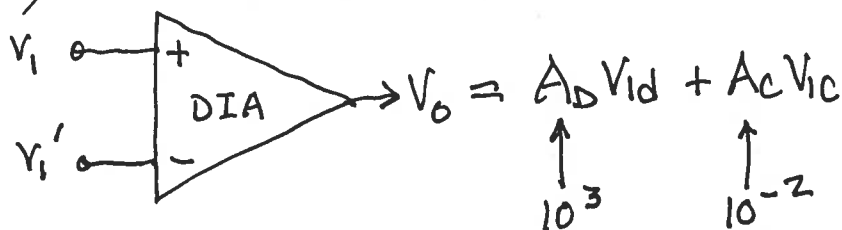

$$\text{A) CMRR}_{\text{dB}} = 20 \log \left( \frac{10^3}{10^{-2}} \right) = \underline{\underline{100\text{dB}}}$$



2.12 B)  $\begin{cases} V_1(t) \equiv 0.002 \sin(2\pi 400t) \\ V_1'(t) = -0.002 \sin(2\pi 400t) + 2 \sin(377t) \end{cases}$   $\swarrow 60\text{Hz HUM}$

$$V_{Id} = \frac{V_1 - V_1'}{2} = 0.002 \sin(2\pi 400t) - 1 \sin(377t)$$

$$V_{Ic} = \frac{V_1 + V_1'}{2} = +1 \sin(377t)$$

$$\therefore V_o(t) = 2 \sin(2\pi 400t) - 10^3 \sin(377t) + 10^{-2} \times 1 \sin(377t)$$

$\downarrow^*$

\* BECAUSE OF HIGH DM HUM COMPONENT, OP AMP SATURATES DUE TO HUM, GET SQ WAVE OUT! IS USELESS.

2.13) A WIEN BRIDGE NOTCH FILTER: (SEE FIG. P 2.13)

$$V_o = (V_3 - V_2), \quad V_1 = K_D(V_o - V_s) = K_D(V_3 - V_2 - V_s)$$

$$\text{BUT } V_2 = V_1 \frac{R}{R+2R} = \frac{V_1}{3}, \quad \therefore V_1 = K_D \left[ V_3 - \frac{V_1}{3} - V_s \right]$$

$$\downarrow$$

$$V_1 \left[ 1 + \frac{K_D}{3} \right] = K_D(V_3 - V_s)$$

$$\text{Now } V_3 = V_1 \frac{\frac{1}{sC + G}}{\frac{1}{sC + G} + R + \frac{1}{sC}}$$

$\downarrow$

$$V_3 = V_1 \frac{sRC}{s(RC)^2 + s3RC + 1}$$

$\Rightarrow$

2.13 A)  $V_o = V_3 - V_2 = V_1 \left[ \frac{sRC}{s^2(RC)^2 + s3RC + 1} - \frac{1}{3} \right]$

$\downarrow$

$$V_o = -K_D [V_o - V_s] \left[ \frac{s^2(RC)^2 + 1}{s^2(RC)^2 + s3RC + 1} \right]$$

$\downarrow$  MORE ALG!

A)  $\frac{V_o}{V_s}(j\omega) = \frac{K_D}{K_D + 1} \frac{(j\omega)^2(RC)^2 + 1}{\left\{ (j\omega)^2(RC)^2 + \frac{3RC}{K_D + 1} j\omega + 1 \right\}}$

B)  $f_n = \frac{\omega_n}{2\pi} = \frac{1}{2\pi RC}$


Let  $C = 10^{-6} F$  (1  $\mu F$ ),  $\therefore R = \frac{1}{377 \times 10^{-6}} = \underline{\underline{2.653 E3 \Omega}}$

C) DC GAIN:  $\omega_n$ :

$A_{V_o} = \frac{K_D}{K_D + 1}$ ,  $\omega_n = \frac{1}{RC}$  r/s,  $\frac{2\xi}{\omega_n} = \frac{3RC}{K_D + 1} \rightarrow 2\xi = \frac{3}{K_D + 1}$   
 $\therefore Q = \frac{1}{2\xi} = \frac{K_D + 1}{3}$

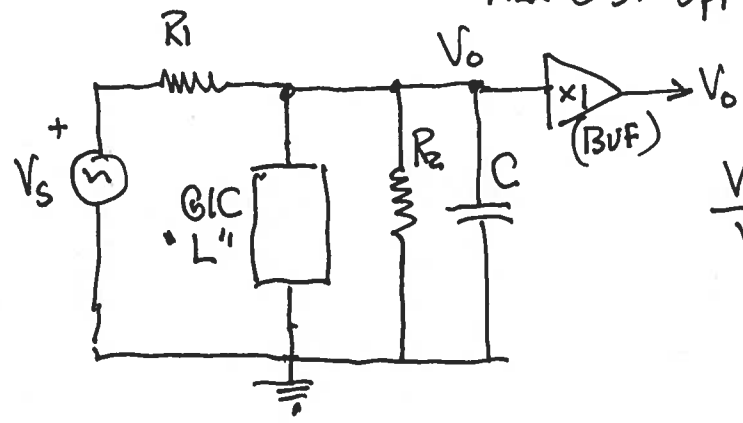2.14) DESIGN A QUADRATIC BPF  $\Sigma$  GIC CKT:

$f_n = 1 Hz$ ,  $Q = 10$ , ALL  $R$ 's:  $10^3 - 10 M$   
 ALL  $C$ 's:  $3 pF - 1 \mu F$




$$\frac{V_o}{V_s}(s) = \frac{1}{\frac{sC + G_2 + 1/sL}{R_1}} = \frac{sL/R_1}{s^2LC + sLG_2 + 1}$$

2.4) GIC "L":

$$\vec{Z}_{11} = \frac{\vec{Z}_1 \vec{Z}_3 \vec{Z}_5}{\vec{Z}_2 \vec{Z}_4}$$

$$\vec{Z}_{11} = \frac{R_1 R_3 R_5}{R_2 \frac{1}{j\omega C_4}}$$
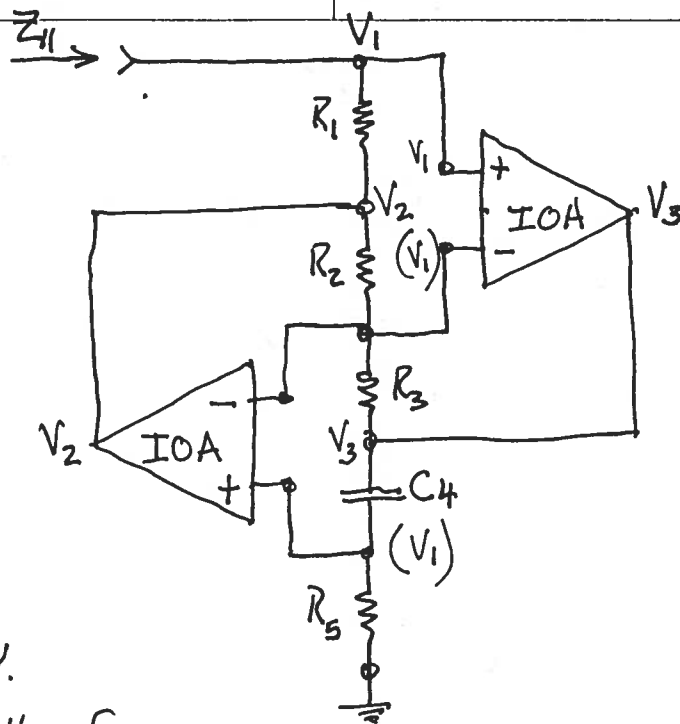
$$\vec{Z}_{11} = j\omega \left[ C_4 \frac{R_1 R_3 R_5}{R_2} \right]$$



$$\therefore L_{eq} = C_4 R_1 R_3 R_5 / R_2 \text{ HY.}$$

\* NEED HUGE  $L_{eq}$  FOR 1 Hz  $f_n$ :

$$L_{eq} = 10^3 \text{ HY} \Rightarrow 10^{-6} \frac{10^4 \times 10^4 \times 10^4}{10^3} = 10^{-6} \times 10^9 = 10^3 \text{ HY}$$

$\uparrow$   $C_4$                        $\leftarrow R_2$

$$Q = \frac{1}{L G_2 \omega_n} = \frac{\sqrt{LC}}{h G_2} \approx 10 \quad \omega_n = \frac{1}{\sqrt{LC}} \text{ r/s}$$

$$100 = \frac{LC}{L^2 G_2^2} \rightarrow G_2^2 = \frac{C}{L} \frac{1}{100} \rightarrow G_2 = \sqrt{\frac{C}{L} \frac{1}{100}}, \therefore R_2 = 10 \sqrt{\frac{L}{C}}$$

$$f_n^2 = 1 = \frac{1}{(2\pi)^2 LC} \rightarrow C = \frac{1}{(2\pi)^2 L} = 2.533 \times 10^{-5} = 25.33 \mu\text{F}$$

$$\therefore R_2 = 10 \sqrt{\frac{10^3}{10^{-6} \times 25.33}} = 6.283 \times 10^4 \Omega \text{ FOR } Q \approx 10$$

\* FOR UNITY GAIN, LET  $R_1 = R_2$

2.15) (SEE FIG. P 2.15)


$$A) \frac{V_o}{V_i}(s) = \frac{-\frac{R_2}{R_1}}{1 + \left[ \left( +\frac{R_2}{R_3} \right) \left( \frac{+V_c}{10} \right) \left( \frac{+1}{sR_4C} \right) \right]} = \frac{-s \frac{R_2}{R_1}}{\left( s + \frac{R_2}{R_3} \frac{V_c}{10} \frac{1}{R_4C} \right)}$$

IN TC FORM:

$$\frac{V_o}{V_i}(s) = \frac{-s \left( \frac{10 R_3 R_4 C}{R_1 V_c} \right)}{\left[ s \left( \frac{10 R_3 R_4 C}{V_c R_2} \right) + 1 \right]}$$

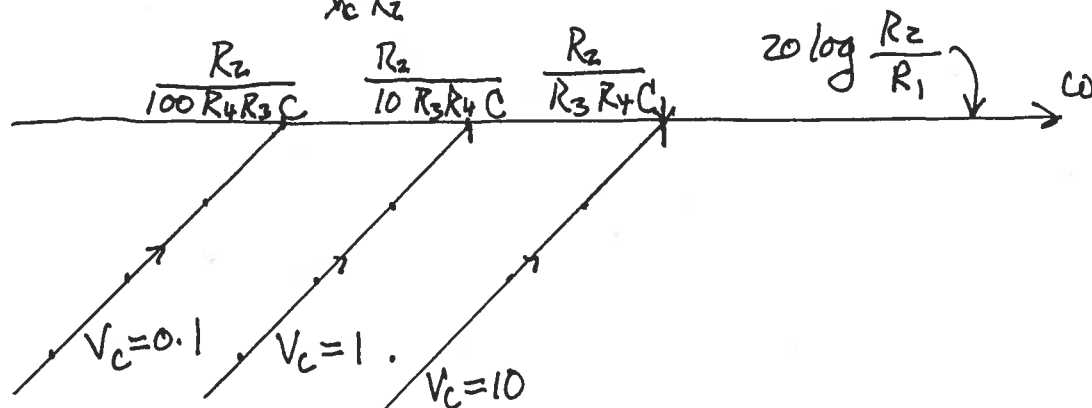B) HI-F. GAIN:

$$\frac{V_o}{V_i}(HI) = \frac{-\frac{R_2}{R_1} \frac{V_c}{V_c}}{\frac{V_c R_2}{V_c R_1}} = -\frac{R_2}{R_1}$$



2.16)  $V_3 = \frac{V_1}{2}$

BY KCL:  $V_2 \left[ G + s2C \right] - V_o sC = V_1 \left[ G + s\frac{C}{2} \right]$

AT THE S.I:  $V_i' \left[ \frac{G}{4} + sC \right] - V_o \frac{G}{4} - V_2 sC = 0$

BUT  $V_i' = V_i = \frac{V_1}{2}$

$$\downarrow \left[ -V_2 sC - V_o \frac{G}{4} = -\frac{V_1}{2} \left[ sC + \frac{G}{4} \right] \right]$$

SOLVE BY  
CRAMER'S RULE:



2.16) FIND:

$$\frac{V_o}{V_i}(s) = \frac{\frac{1}{2} [1 - sZRC + s^2(ZRC)^2]}{[1 + sZRC + s^2(ZRC)^2]}, \quad \omega_n = \frac{1}{ZRC} \text{ rad/s}$$

$$\frac{2\zeta}{\omega_n} = ZRC \rightarrow \zeta = \frac{ZRC}{2} \frac{1}{ZRC} = \frac{1}{2}$$

\* THIS IS AN ALL-PASS FILTER.

2.17) @ S.I. OF IOA-1:

$$\cancel{V_i} [G_1 + G_1 + G_2] - G_1 \frac{V_2^2}{\cancel{V_i}} - G_1 \frac{V_1^2}{\cancel{V_i}} - G_2 \left( \frac{-V_o^2}{\cancel{V_i}} \right) = 0$$

$$G_1(V_2^2 + V_1^2) = G_2 V_o^2$$



$$V_o^2 = \frac{G_1}{G_2} (V_2^2 + V_1^2)$$

$$V_o = \sqrt{\frac{R_2}{R_1}} \sqrt{V_2^2 + V_1^2}$$

{ NEED INVERTER TO SUM IS  
CORRECTLY @ IOA-1 S.I. }

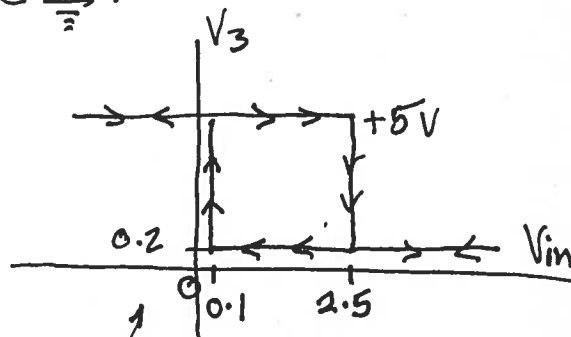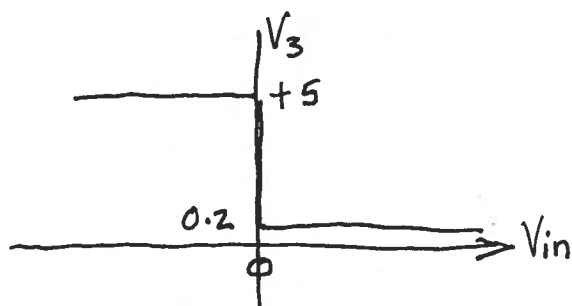2.18) A)  $V_B = f(V_{in}, R_1, R_2)$ ?  $V_B \equiv 0$

WITH NO  $R_1, R_2$  FEEDBACK:  $V_2 @ \frac{1}{3}$ .




WITH FEEDBACK, GET HYSTERESIS:


$$\text{KCL @ } V_2 \text{ NODE: } V_2 [G_1 + G_2] - V_3 G_2 = 0 \rightarrow V_2 = \frac{V_3 R_1}{R_1 + R_2} \Rightarrow$$

$$2.18) \begin{cases} \text{For } V_3 \text{ TO } 00 \text{ LO; } V_1 = \frac{5R_1}{R_1 + R_3} = \frac{5 \times 100K}{200K} = 2.5 = V_{in} \\ \text{For } V_3 \text{ TO } 00 \text{ HI; } V_1 \leq \frac{0.2 \times 100K}{200K} = 0.1V. = V_{in} \end{cases}$$

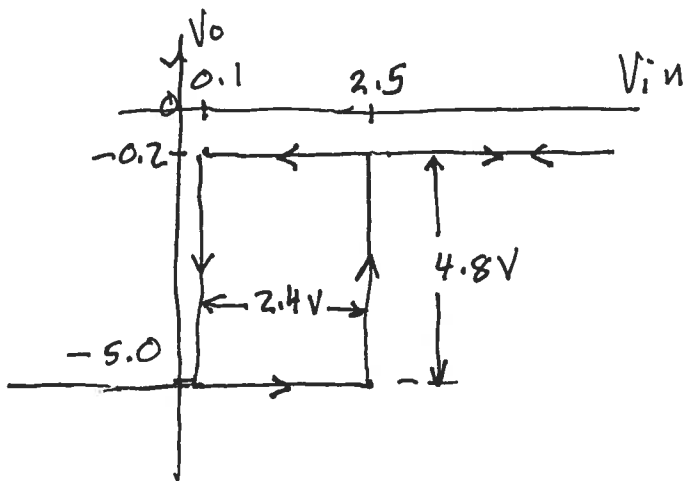B) THE IOA INVERTS  $V_3$ :  
i.e.,  $V_o = -V_3$



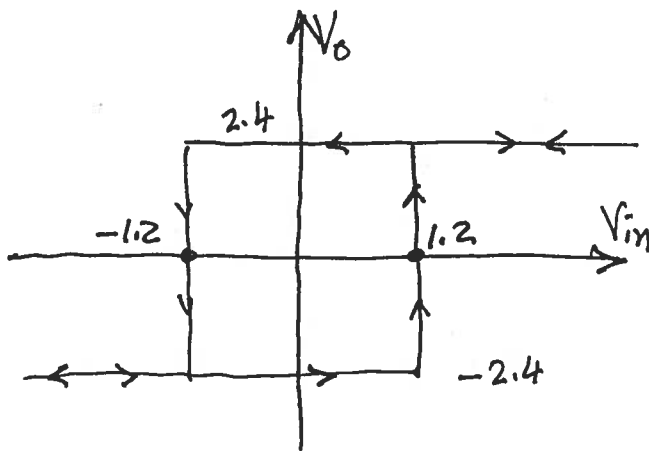c) TO MAKE HYST. LOOP CENTERED ON  $0,0$ :



ADD +2.6 V TO RAISE:

$$\therefore V_C = -2.6$$

$$V_B + 2.5 = 1.2$$

$$\therefore \underline{V_B = -1.3}$$