



Figure B.1 Schematics of various switches. (a) Single-pole single throw. (b) Single-pole double throw. (c) Double-pole single throw. (d) Double-pole double throw. (e) Double-cross switch.